

9.1

$$\left. \begin{array}{l} A_v = -\frac{200}{20} = -10 \\ \text{and} \\ R_i = 20 \text{ k}\Omega \end{array} \right\} \text{for each case}$$

9.2

a.  $A_v = -\frac{100}{10} = -10$

$$R_i = R_1 = 10 \text{ k}\Omega$$

b.  $A_v = -\frac{100 \parallel 100}{10} = -5$

$$R_i = R_1 = 10 \text{ k}\Omega$$

c.  $A_v = -\frac{100}{10+10} = -5$

$$R_i = 10+10 = 20 \text{ k}\Omega$$

9.3

$$A_v = -\frac{R_2}{R_1} = -12 \Rightarrow R_2 = 12R_1$$

$$R_i = R_1 = 25 \text{ k}\Omega$$

$$\Rightarrow \underline{R_2 = (12)(25) = 300 \text{ k}\Omega}$$

9.4

$$A_v = -\frac{R_2}{R_1} = -8 \Rightarrow R_2 = 8R_1$$

$$\text{For } v_T = -1, i_1 = \frac{1}{R_1} = 15 \mu\text{A} \Rightarrow \underline{R_1 = 66.7 \text{ k}\Omega}$$

$$\Rightarrow \underline{R_2 = 533.3 \text{ k}\Omega}$$

9.29

$$v_o = \left(1 + \frac{50}{50}\right) \left[ \left(\frac{20}{20+40}\right) v_{I2} + \left(\frac{40}{20+40}\right) v_{I1} \right]$$

$$\underline{v_o = 1.33v_{I1} + 0.667v_{I2}}$$

9.30


$$v_o = \left(1 + \frac{100}{50}\right)$$

$$\times \left[ \left(\frac{10 \parallel 40}{10 \parallel 40 + 20}\right) v_{I1} + \left(\frac{10 \parallel 20}{10 \parallel 20 + 40}\right) v_{I2} \right]$$

$$v_o = 3 \left[ \left(\frac{8}{8+20}\right) v_{I1} + \left(\frac{6.67}{6.67+40}\right) v_{I2} \right]$$

$$\underline{v_o = 0.857v_{I1} + 0.429v_{I2}}$$

9.31

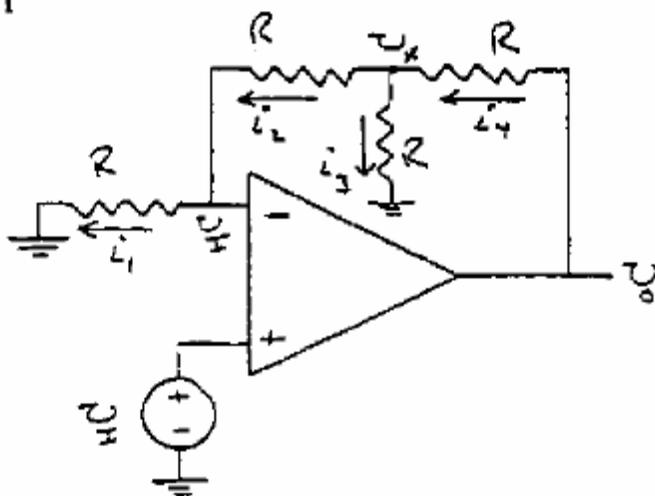

$$i_1 = \frac{v_I}{R} = i_2$$

$$v_X = i_2 R + v_I = \left(\frac{v_I}{R}\right) R + v_I = 2v_I$$

$$i_3 = \frac{v_X}{R} = \frac{2v_I}{R}$$

$$i_4 = i_2 + i_3 = \frac{v_I}{R} + \frac{2v_I}{R} = \frac{3v_I}{R}$$

$$v_o = i_4 R + v_X = \left(\frac{3v_I}{R}\right) R + 2v_I$$

$$\underline{\frac{v_o}{v_I} = 5}$$

9.34

$$v_{o1} = \left(1 + \frac{R_2}{R_1}\right) v_I$$

$$v_{o1} = \left(1 + \frac{R_2}{R_1}\right) v_I, \quad v_{o2} = -\left(1 + \frac{R_2}{R_1}\right) v_I$$

$$\text{So } \underline{v_{o1} = -v_{o2}}$$

9.36

$$(a) \quad v_x = \left(\frac{20}{20+40}\right) \cdot v_I = \left(\frac{20}{60}\right)(6) = 2$$

$$\underline{v_o = 2 V}$$

(b) Same as (a)

$$(c) \quad v_x = \left(\frac{6}{6+48}\right)(6) = 0.666 V$$

$$v_o = \left(1 + \frac{10}{10}\right) \cdot v_x \Rightarrow \underline{v_o = 1.33 V}$$