

15.36

$$a. \quad V_{TH} = \left( \frac{R_1}{R_1 + R_2} \right) V_H = \left( \frac{10}{10 + 40} \right) (10)$$

$$\text{so } \underline{V_{TH} = 2 \text{ V}}$$

$$V_{TL} = \left( \frac{R_1}{R_1 + R_2} \right) V_L = \left( \frac{10}{10 + 40} \right) (-10)$$

$$\text{so } \underline{V_{TL} = -2 \text{ V}}$$

$$b. \quad v_I = 5 \sin \omega t$$

15.37

a. Upper crossover voltage when  $v_o = +V_P$ .

Now

$$v_B = \left( \frac{R_1}{R_1 + R_2} \right) (+V_P)$$

and

$$v_A = \left( \frac{R_A}{R_A + R_B} \right) V_{REF} + \left( \frac{R_B}{R_A + R_B} \right) V_{TH}$$

$v_A = v_B$  so that

$$\begin{aligned} & \left( \frac{R_1}{R_1 + R_2} \right) V_P \\ &= \left( \frac{R_A}{R_A + R_B} \right) V_{REF} + \left( \frac{R_B}{R_A + R_B} \right) V_{TH} \end{aligned}$$

or

$$V_{TH} = \left( \frac{R_A + R_B}{R_1 + R_2} \right) \left( \frac{R_1}{R_B} \right) V_P - \left( \frac{R_A}{R_B} \right) V_{REF}$$

Lower crossover voltage when  $v_o = -V_P$

So

$$V_{TL} = - \left( \frac{R_A + R_B}{R_1 + R_2} \right) \left( \frac{R_1}{R_B} \right) V_P - \left( \frac{R_A}{R_B} \right) V_{REF}$$

$$b. \quad V_{TH} = \left( \frac{10 + 20}{5 + 20} \right) \left( \frac{5}{20} \right) (10) - \left( \frac{10}{20} \right) (2)$$

$$\text{or } \underline{V_{TH} = 2 \text{ V}}$$

and

$$V_{TL} = - \left( \frac{10 + 20}{5 + 20} \right) \left( \frac{5}{20} \right) (10) - 1 \Rightarrow \underline{V_{TL} = -4 \text{ V}}$$

15.38

$$\begin{aligned}
 \text{a. } \frac{v_B}{R_1} &= \frac{V_{REF} - v_B}{R_3} + \frac{v_0 - v_B}{R_2} \\
 v_B \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) &= \frac{V_{REF}}{R_3} + \frac{v_0}{R_2} \\
 V_{TH} = v_B \text{ when } v_0 = +V_P \text{ and } V_{TL} = v_B \text{ when } \\
 v_0 = -V_P
 \end{aligned}$$

So

$$V_{TH} = \frac{\frac{V_{REF}}{R_3} + \frac{V_P}{R_2}}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

and

$$V_{TL} = \frac{\frac{V_{REF}}{R_3} - \frac{V_P}{R_2}}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

b.

$$\begin{aligned}
 V_S &= \frac{V_{REF}}{R_3 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} \\
 -5 &= \frac{-10}{10 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{10} \right)}
 \end{aligned}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{5} - \frac{1}{10} = 0.10$$

$$\Delta V_T = V_{TH} - V_{TL} = \frac{\frac{2V_P}{R_2}}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

$$0.2 = \frac{2(12)}{R_2(0.10 + 0.10)}$$

$$\text{So } \underline{R_2 = 600 \text{ k}\Omega}$$

Then

$$\frac{1}{R_1} + \frac{1}{R_2} = 0.10$$

$$\frac{1}{R_1} + \frac{1}{600} = 0.10 \Rightarrow \underline{R_1 = 10.17 \text{ k}\Omega}$$

$$\text{c. } V_{TH} = -5 + 0.1 = -4.9$$

$$V_{TL} = -5 - 0.1 = -5.1$$

15.40

a. Switching point is when  $v_0 = 0$ . Then

$$v_+ = v_- \equiv V_S = \left( \frac{R_2}{R_1 + R_2} \right) V_{REF}$$

$V_{TH}$  occurs when  $v_0 = V_H$ , then by superposition

$$v_+ = V_{TH} = \left( \frac{R_1}{R_1 + R_2} \right) V_H + \left( \frac{R_2}{R_1 + R_2} \right) V_{REF}$$

or

$$V_{TH} = V_S + \left( \frac{R_1}{R_1 + R_2} \right) V_H$$

$V_{TL}$  occurs when  $v_0 = V_L$ , then by superposition

$$v_+ = V_{TL} = \left( \frac{R_1}{R_1 + R_2} \right) V_L + \left( \frac{R_2}{R_1 + R_2} \right) V_{REF}$$

or

$$V_{TL} = V_S + \left( \frac{R_1}{R_1 + R_2} \right) V_L$$

b. For  $V_{TH} = 2$  V and  $V_{TL} = 1$  V, then  $V_S = 1.5$  V

Now

$$2 = 1.5 + \left( \frac{10}{10 + R_2} \right) (10)$$

$$\frac{0.5}{10} = \frac{10}{10 + R_2} \Rightarrow \underline{R_2 = 190 \text{ k}\Omega}$$

$$\text{Now } V_S = 1.5 = \left( \frac{190}{10 + 190} \right) V_{REF}$$

so

$$\underline{V_{REF} = 1.579 \text{ V}}$$

15.41

a. Switching point when  $v_o = 0$ .

Now

$$v_+ = V_{REF} = \left( \frac{R_2}{R_1 + R_2} \right) v_I \text{ where } v_I = V_S.$$

Then

$$V_S = \left( \frac{R_1 + R_2}{R_2} \right) V_{REF} = \left( 1 + \frac{R_1}{R_2} \right) V_{REF}$$

Now upper crossover voltage for  $v_I$  occurs when  $v_o = V_L$  and  $v_+ = V_{REF}$ . Then

$$\frac{V_{TH} - V_{REF}}{R_1} = \frac{V_{REF} - V_L}{R_2}$$

$$\text{or } V_{TH} = -\frac{R_1}{R_2} \cdot V_L + V_{REF} \left( 1 + \frac{R_1}{R_2} \right)$$

$$\text{or } V_{TH} = V_S - \frac{R_1}{R_2} \cdot V_L$$

Lower crossover voltage for  $v_I$  occurs when  $v_o = V_H$  and  $v_+ = V_{REF}$ . Then

$$\frac{V_H - V_{REF}}{R_2} = \frac{V_{REF} - V_{TL}}{R_1}$$

$$\text{or } V_{TL} = -\frac{R_1}{R_2} \cdot V_H + V_{REF} \left( 1 + \frac{R_1}{R_2} \right)$$

$$\text{or } V_{TL} = V_S - \frac{R_1}{R_2} \cdot V_H$$

b. For  $V_{TH} = -1$  and  $V_{TL} = -2$ ,  $V_S = -1.5$  V.

$$\text{Then } V_{TL} = V_S - \frac{R_1}{R_2} \cdot V_H \Rightarrow -2 = -1.5 - \frac{R_1}{20} \quad (12)$$

so that  $R_1 = 0.833 \text{ k}\Omega$

Now

$$V_S = \left( 1 + \frac{R_1}{R_2} \right) V_{REF}$$

$$-1.5 = \left( 1 + \frac{0.833}{20} \right) V_{REF}$$

which gives

$$\underline{V_{REF} = -1.44 \text{ V}}$$