

15.50

a. Switching voltage

$$v_X = \left( \frac{R_1 + R_3}{R_1 + R_3 + R_2} \right) \cdot V_P = \left( \frac{10 + 10}{10 + 10 + 10} \right) (\pm 10)$$

$$\text{So } v_X = \pm 6.667 \text{ V}$$

Using Equation (15.83(b))

$$v_X = V_P + \left( -\frac{2}{3}V_P - V_P \right) e^{-t_1/\tau_X} = \frac{2}{3}V_P$$

$$\text{Then } 1 - \frac{5}{3} \cdot e^{-t_1/\tau_X} = \frac{2}{3}$$

$$\frac{1}{3} = \frac{5}{3} \cdot e^{-t_1/\tau_X} \text{ or } t_1 = \tau_X \ln(5)$$

$$t_1 = \frac{T}{2} = \frac{1}{2f} = \frac{1}{2(500)} \Rightarrow t_1 = 0.001 \text{ s}$$

$$10^{-3} = \tau_X \ln(5) \Rightarrow \tau_X = 6.21 \times 10^{-4} \\ = R_X(0.01 \times 10^{-6})$$

$$\text{So } \underline{R_X = 62.1 \text{ k}\Omega}$$

b. Switching voltage

$$v_X = \left( \frac{R_1}{R_1 + R_3 + R_2} \right) (\pm V_P) \\ = \left( \frac{10}{10 + 10 + 10} \right) (\pm V_P) = \frac{1}{3} \cdot (\pm V_P)$$

Using Equation (15.83(b))

$$v_X = V_P + \left( -\frac{1}{3}V_P - V_P \right) e^{-t_1/\tau_X} = \frac{1}{3}V_P$$

$$\text{Then } 1 - \frac{4}{3} \cdot e^{-t_1/\tau_X} = \frac{1}{3}$$

$$\frac{2}{3} = \frac{4}{3} \cdot e^{-t_1/\tau_X}$$

$$t_1 = \tau_X \ln(2) = (6.21 \times 10^{-4}) \ln(2) = 4.30 \times 10^{-4} \text{ s}$$

$$T = 2t_1 = 8.6 \times 10^{-4} \text{ s}$$

$$f = \frac{1}{T} \Rightarrow \underline{f = 1.16 \text{ kHz}}$$

15.53

a. From Equation (15.95)

$$T = 1.1RC$$

$$\text{For } T = 60 \text{ s} = 1.1RC$$

$$\text{then } RC = 54.55 \text{ s}$$

For example, let

$$\underline{C = 50 \mu\text{F}} \text{ and } \underline{R = 1.09 \text{ M}\Omega}$$

b. Recovery time: capacitor is discharged by current through the discharge transistor.

$$\text{If } V^+ = 5 \text{ V, then } I_B \approx \frac{5 - 0.7}{100} = 0.043 \text{ mA}$$

$$\text{If } \beta = 100, I_C = 4.3 \text{ mA}$$

$$V_C = \frac{1}{C} \int I_C dt = \frac{I_C}{C} \cdot t$$

$$\text{Capacitor has charged to } \frac{2}{3} \cdot V^+ = 3.33 \text{ V}$$

$$\text{So that } t = \frac{V_C \cdot C}{I_C} = \frac{(3.33)(50 \times 10^{-6})}{4.3 \times 10^{-3}}$$

$$\text{So recovery time } \underline{t \approx 38.7 \text{ ms}}$$

15.54

$$T = 1.1RC$$

$$5 \times 10^{-6} = 1.1RC$$

$$\text{so } RC = 4.545 \times 10^{-6} \text{ s}$$

For example, let

$$\underline{C = 100 \text{ pF}} \text{ and } \underline{R = 45.5 \text{ k}\Omega}$$

From Problem (15.53), recovery time

$$t \approx \frac{V_C \cdot C}{I_C} = \frac{(3.33)(100 \times 10^{-12})}{4.3 \times 10^{-3}}$$

or

$$\underline{t = 77.4 \text{ ns}}$$

15.55

From Equation (15.102),

$$f = \frac{1}{(0.693)(20 + 2(20)) \times 10^3 \times (0.1 \times 10^{-6})}$$

$$\text{or } f = 240.5 \text{ Hz}$$

$$\text{Duty cycle} = \frac{20 + 20}{20 + 2(20)} \times 100\% = \underline{66.7\%}$$

15.56

$$f = \frac{1}{(0.693)(R_A + 2R_B)C}$$

$$R_A = R_1 = 10 \text{ k}\Omega, R_B = R_2 + \alpha R_3$$

$$\text{So } 10 \text{ k}\Omega \leq R_B \leq 110 \text{ k}\Omega$$

$$f_{\min} = \frac{1}{(0.693)(10 + 2(110)) \times 10^3 \times (0.01 \times 10^{-6})}$$
$$= 627 \text{ Hz}$$

$$f_{\max} = \frac{1}{(0.693)(10 + 2(10)) \times 10^3 \times (0.01 \times 10^{-6})}$$
$$= 4.81 \text{ kHz}$$

$$\text{So } 627 \text{ Hz} \leq f \leq 4.81 \text{ kHz}$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

Now

$$\frac{10 + 10}{10 + 2(10)} \times 100\% = \underline{66.7\%}$$

and

$$\frac{10 + 110}{10 + 2(110)} \times 100\% = \underline{52.2\%}$$

$$\text{So } 52.2 \leq \text{Duty cycle} \leq 66.7\%$$

15.57

$$1 \text{ k}\Omega \leq R_A \leq 51 \text{ k}\Omega$$

$$1 \text{ k}\Omega \leq R_B \leq 51 \text{ k}\Omega$$

$$f_{\min} = \frac{1}{(0.693)(1 + 2(51)) \times 10^3 \times (0.01 \times 10^{-6})}$$
$$= 1.40 \text{ kHz}$$

$$f_{\max} = \frac{1}{(0.693)(51 + 2(1)) \times 10^3 \times (0.01 \times 10^{-6})}$$
$$= 2.72 \text{ kHz}$$

$$\text{or } 1.40 \text{ kHz} \leq f \leq 2.72 \text{ kHz}$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$\frac{1 + 51}{1 + 2(51)} \times 100\% = \underline{50.5\%}$$

or

$$\frac{51 + 1}{51 + 2(1)} \times 100\% = \underline{98.1\%}$$

$$\text{or } \underline{50.5\% \leq \text{Duty cycle} \leq 98.1\%}$$