

2.1 Prove the following theorems algebraically:

- (a)  $X(X' + Y) = XY$       (b)  $X + XY = X$   
 (c)  $XY + XY' = X$       (d)  $(A + B)(A + B') = A$

2.2 Illustrate the following theorems using circuits of switches:



- (a)  $X + XY = X$       (b)  $X + YZ = (X + Y)(X + Z)$

In each case, explain why the circuits are equivalent.

2.3 Simplify each of the following expressions by applying *one* of the theorems. State the theorem used (see page 55).

- (a)  $X'Y'Z + (X'Y'Z)'$       (b)  $(AB' + CD)(B'E + CD)$   
 (c)  $ACF + AC'F$       (d)  $A(C + D'B) + A'$   
 (e)  $(A'B + C + D)(A'B + D)$       (f)  $(A + BC) + (DE + F)(A + BC)'$

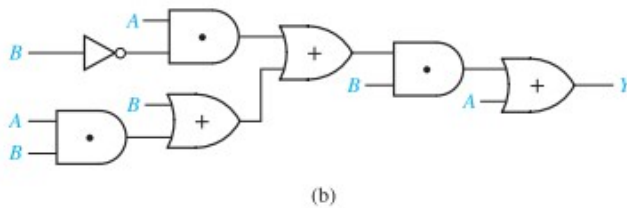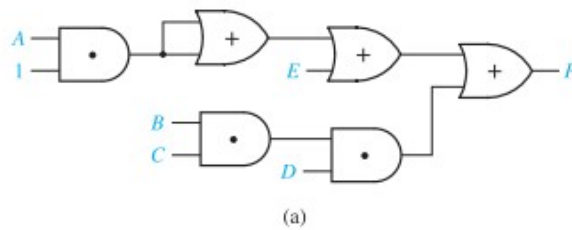2.4 For each of the following circuits, find the output and design a simpler circuit having the same output. (*Hint*: Find the circuit output by first finding the output of each gate, going from left to right, and simplifying as you go.)



2.5 Multiply out and simplify to obtain a sum of products:

- (a)  $(A + B)(C + B)(D' + B)(ACD' + E)$   
 (b)  $(A' + B + C')(A' + C' + D)(B' + D')$

2.6 Factor each of the following expressions to obtain a product of sums:

- (a)  $AB + C'D'$       (b)  $WX + WY'X + ZYX$   
 (c)  $A'BC + EF + DEF'$       (d)  $XYZ + W'Z + XQ'Z$   
 (e)  $ACD' + C'D' + A'C$       (f)  $A + BC + DE$

(The answer to (f) should be the product of four terms, each a sum of three variables.)

2.7 Draw a circuit that uses only one AND gate and one OR gate to realize each of the following functions:


(a)  $(A + B + C + D)(A + B + C + E)(A + B + C + F)$

(b)  $WXYZ + VXYZ + UXYZ$


2.8 Simplify the following expressions to a minimum sum of products.

(a)  $[(AB)' + C'D]'$       (b)  $[A + B(C' + D)]'$       (c)  $((A + B')C')(A + B)(C + A)'$

2.9 Find  $F$  and  $G$  and simplify:

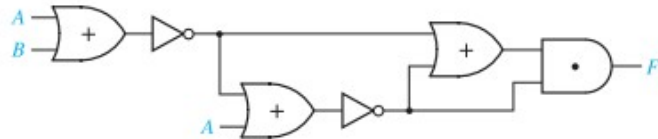

(a)

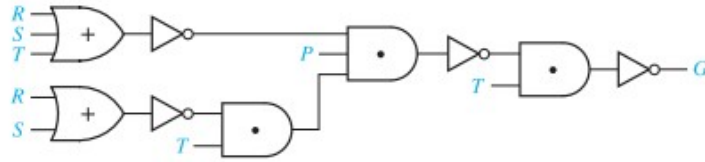

(b)



