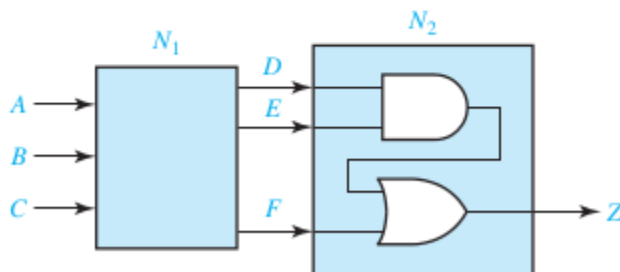


- 4.3** Given  $F_1 = \sum m(0, 4, 5, 6)$  and  $F_2 = \sum m(0, 3, 6, 7)$  find the minterm expression for  $F_1 + F_2$ . State a general rule for finding the expression for  $F_1 + F_2$  given the minterm expansions for  $F_1$  and  $F_2$ . Prove your answer by using the general form of the minterm expansion.
- 4.4** (a) How many switching functions of two variables ( $x$  and  $y$ ) are there?  
 (b) Give each function in truth table form and in reduced algebraic form.
- 4.5** A combinational circuit is divided into two subcircuits  $N_1$  and  $N_2$  as shown. The truth table for  $N_1$  is given. Assume that the input combinations  $ABC = 110$  and  $ABC = 010$  never occur. Change as many of the values of  $D$ ,  $E$ , and  $F$  to don't-cares as you can without changing the value of the output  $Z$ .



A	B	C	D	E	F
0	0	0	1	1	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	0	1	0
1	1	1	0	0	0

- 4.9** Given:  $F(a, b, c) = abc' + b'$ .
- (a) Express  $F$  as a minterm expansion. (Use  $m$ -notation.)  
 (b) Express  $F$  as a maxterm expansion. (Use  $M$ -notation.)  
 (c) Express  $F'$  as a minterm expansion. (Use  $m$ -notation.)  
 (d) Express  $F'$  as a maxterm expansion. (Use  $M$ -notation.)
- 4.13** A combinational logic circuit has four inputs ( $A$ ,  $B$ ,  $C$ , and  $D$ ) and one output  $Z$ . The output is 1 iff the input has three consecutive 0's or three consecutive 1's. For example, if  $A = 1, B = 0, C = 0$ , and  $D = 0$ , then  $Z = 1$ , but if  $A = 0, B = 1, C = 0$ , and  $D = 0$ , then  $Z = 0$ . Design the circuit using one four-input OR gate and four three-input AND gates.
- 4.20** A bank vault has three locks with a different key for each lock. Each key is owned by a different person. To open the door, at least two people must insert their keys into the assigned locks. The signal lines  $A$ ,  $B$ , and  $C$  are 1 if there is a key inserted into lock 1, 2, or 3, respectively. Write an equation for the variable  $Z$  which is 1 iff the door should open.


**4.29** Find both the minterm expansion and maxterm expansion for the following functions, using *algebraic manipulations*:

(a)  $f(A, B, C, D) = AB + A'CD$

(b)  $f(A, B, C, D) = (A + B + D')(A' + C)(C + D)$

**7.8** (a) Convert the following circuit to all NAND gates, by adding bubbles and inverters where necessary.

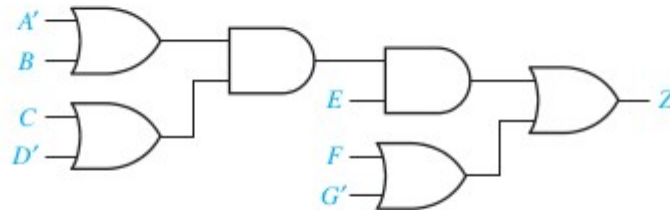(b) Convert to all NOR gates (an inverter at the output is allowed).



**7.9** Find a two-level, multiple-output AND-OR gate circuit to realize the following functions. Minimize the required number of gates (six gates minimum).

$$f_1 = ac + ad + b'd \quad \text{and} \quad f_2 = a'b' + a'd' + cd'$$

**7.22** A combinational switching circuit has four inputs and one output as shown.  $F = 0$  iff three or four of the inputs are 1.

(a) Write the maxterm expansion for  $F$ .

(b) Using AND and OR gates, find a minimum three-level circuit to realize  $F$  (5 gates, 12 inputs).

