 



8.1 Complete the timing diagram for the given circuit. Assume that both gates have a propagation delay of 5 ns.



9.15 Show how to make a 4-to-1 MUX, using an 8-to-1 MUX.


9.16 Implement a 32-to-1 multiplexer using two 16-to-1 multiplexers and a 2-to-1 multiplexer in two ways: (a) Connect the most significant select line to the 2-to-1 multiplexer, and (b) connect the least significant select line to the 2-to-1 multiplexer.

 11.2 A latch can be constructed from an OR gate, an AND gate, and an inverter connected as follows:



- (a) What restriction must be placed on R and H so that P will always equal Q' (under steady-state conditions)?
- (b) Construct a next-state table and derive the characteristic (next-state) equation for the latch.

 
(c) Complete the following timing diagram for the latch.




**11.10** Convert by adding external gates:

- a D flip-flop to a J-K flip-flop.
- a T flip-flop to a D flip-flop.
- a T flip-flop to a D flip-flop with clock enable.

 **11.11** Complete the following timing diagram for an S-R latch. Assume  $Q$  begins at 1.



 **11.12** Using a truth table similar to Figure 11-8(b), confirm that each of these circuits is an S-R latch. What happens when  $S = R = 1$  for each circuit?



- 11.14**
- Construct a state table for this circuit and identify the stable states of the circuit.
  - Derive a Boolean algebra equation for the next value of the output  $Q$  in terms of  $Q$ ,  $A$  and  $B$ .
  - Analyze the behavior of the circuit. Is it a useful circuit? If not, explain why not; if yes, explain what it does.

