

11.16 (a) $Q^+ = AB + QB$


11.16 (c) $AB = 01$ is a hold input combination, $AB = 00$ and 10 are reset input combinations, and $AB = 11$ is a set input combination. This is reset dominant latch where $S = A$ and $R = B'$. $P = Q' + B'$. In each stable state $P = Q'$ even for the input combination $AB = 10$ ($SR = 11$) so P is usable as Q' . Allowing the input combination $AB = 10$ ($SR = 11$) would result in unreliable operation if both A and B could change at the same time, i.e., change to $AB = 01$ ($SR = 00$), because the latch could end up in either state 0 or 1 depending upon the delays in the circuit.

11.16 (b)


Present State Q	Next State Q^+			
	A B		11	10
0	0	0	1	0
1	0	1	1	0

The stable states are in bold.

11.18

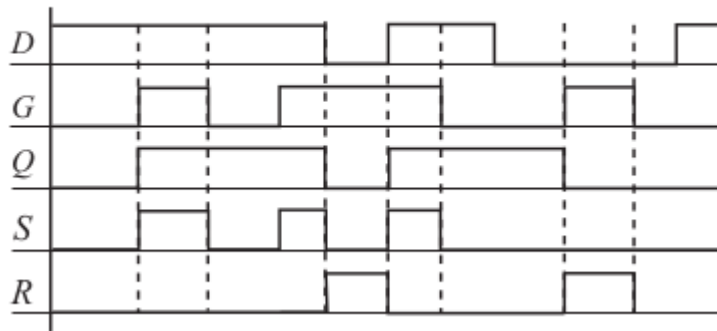


11.27 (a)

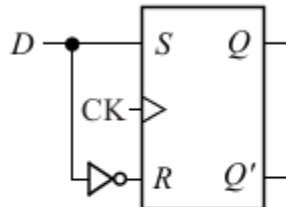


When $D = 0$, then $S = 0$, and $R = 1$, so $Q^+ = 0$.
 When $D = 1$, then $S = 1$, and $R = 0$, so $Q^+ = 1$.

11.27 (a)



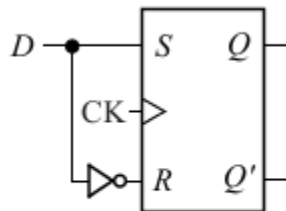


When $D = 0$, then $S = 0$, and $R = 1$, so $Q^+ = 0$.
 When $D = 1$, then $S = 1$, and $R = 0$, so $Q^+ = 1$.

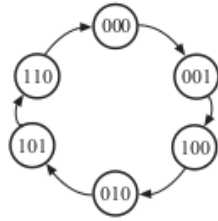12.6 In the following state graph, the first flip-flop (C) takes on the required sequence 0, 0, 1, 0, 1, 1, 1, (repeat).






C B A	C ⁺ B ⁺ A ⁺
0 0 0	0 0 1
0 0 1	1 0 0
0 1 0	1 0 1
0 1 1	X X X
1 0 0	0 1 0
1 0 1	1 1 0
1 1 0	0 0 0
1 1 1	X X X

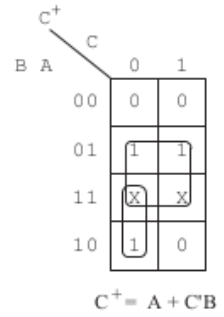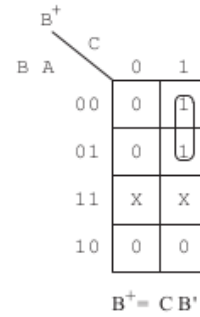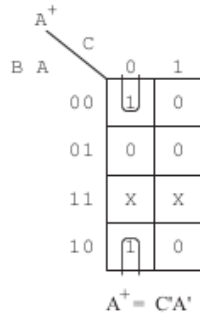




12.7 (a)

C B A	C ⁺ B ⁺ A ⁺
0 0 0	X X X
0 0 1	0 1 1
0 1 0	1 1 0
0 1 1	0 1 0
1 0 0	0 0 1
1 0 1	1 0 0
1 1 0	1 1 1
1 1 1	1 0 1

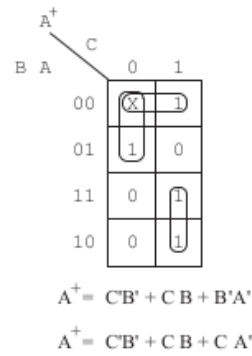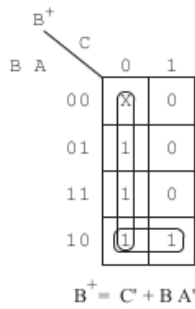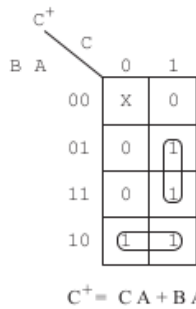

For D flip-flop: 000 goes to 011 because $D_C D_B D_A = 011$

12.7 (b)

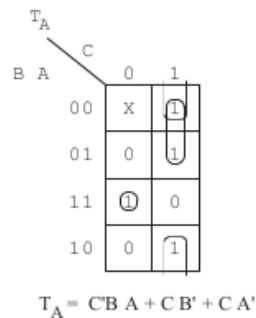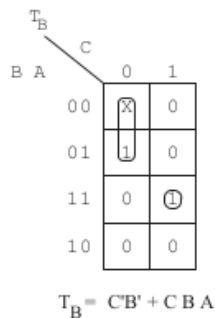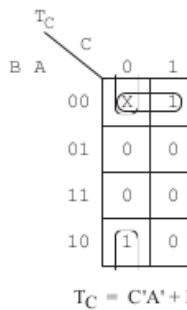

For T flip-flop: 000 goes to 110 because $T_A T_B T_C = 110$

12.8 (a)

CBA	$C^*B^*A^*$
000	XXX
001	011
010	110
011	010
100	001
101	100
110	111
111	101

C^+

$B A$	C	0	1
00		x	0
01		0	1
11		0	1
10		1	1

B^+

$B A$	C	0	1
00		x	0
01		1	0
11		1	0
10		1	1

A^+

$B A$	C	0	1
00		x	1
01		1	0
11		0	1
10		0	1

J_C

$B A$	C	0	1
00		x	x
01		0	x
11		0	x
10		1	x

K_C

$B A$	C	0	1
00		x	1
01		x	0
11		x	0
10		x	0

J_B

$B A$	C	0	1
00		x	0
01		1	0
11		x	x
10		x	x

K_B

$B A$	C	0	1
00		x	x
01		x	x
11		0	1
10		0	0

J_A

$B A$	C	0	1
00		x	1
01		x	x
11		x	x
10		0	1

K_A

$B A$	C	0	1
00		x	x
01		0	1
11		1	0
10		x	x

$J_C = A'$

$K_C = B'A'$

$J_B = C'$

$K_B = CA$

$J_A = C$

$K_A = C'B + CB'$

In state 000,

$J_C = A' = 1, K_C = B'A' = 1, C^+ = C' = 1$

$J_B = C' = 1, K_B = CA = 0, B^+ = 1$

$J_A = C = 0, K_A = C'B + C'B' = 0, A^+ = A = 0$

So the next state is $C^*B^*A^* = 110$

12.8 (b)

S_C

$B A$	C	0	1
00		x	0
01		0	x
11		0	x
10		1	x

R_C

$B A$	C	0	1
00		x	1
01		x	0
11		x	0
10		0	0

S_B

$B A$	C	0	1
00		x	0
01		1	0
11		x	0
10		x	x

R_B

$B A$	C	0	1
00		x	x
01		0	x
11		0	1
10		0	0

S_A

$B A$	C	0	1
00		x	1
01		x	0
11		0	x
10		0	1

R_A

$B A$	C	0	1
00		x	0
01		0	1
11		1	0
10		x	0

$S_C = BA'$

$R_C = B'A'$

$S_B = C'$

$R_B = CA$

$S_A = CA'$

$R_A = C'B + C'B'$

$S_C = C'A'$

In state 000,

$S_C = BA' = 0, R_C = B'A' = 1, C^+ = 0$

$S_B = C' = 1, R_B = CA = 0, B^+ = 1$

$S_A = CA' = 0, R_A = C'B + C'B' = 0, A^+ = A = 0$

So the next state is $C^*B^*A^* = 010$

12.19

ABC	$A'B'C'$
000	XXX
001	100
010	011
011	001
100	101
101	111
110	010
111	110

12.19 (a) $D_A = B' + AC$; $D_B = AC + BC'$; $D_C = A'B + AB'$

12.19 (b) $J_A = B'$, $K_A = BC'$; $J_B = AC$, $K_B = A'C$; $J_C = A' + B'$, $K_C = A'B' + AB$

12.19 (c) $T_A = A'B' + ABC'$; $T_B = A'BC + AB'C$; $T_C = A'B' + A'C' + B'C' + ABC$

12.19 (d) $S_A = B'$, $R_A = BC'$; $S_B = AC$, $R_B = A'C$; $S_C = A'B + AB'$, $R_C = A'B' + AB$

12.19 (e) State 000 goes to 100, because $D_A D_B D_C = 100$.