
EEL 4783: HDL in Digital System Design

Lecture 1: Introduction*

Prof. Mingjie Lin



Overview

- What is an digital embedded system?
- Why HDL (Hardware Description Language)?
- Why take this course?
- Class mechanics
 - Administrative issues
 - Lecture topics
 - Assignment and projects

What is an Digital Embedded System?

- ES from 10,000 Feet Above
 - a computer system designed for specific control functions within a larger system
 - often with real-time computing constraints
 - embedded as part of a complete device often including hardware and mechanical parts
- By contrast, a general-purpose computer
 - designed to be flexible and to meet a wide range of end-user needs

Embedded Computing Systems

- Obvious examples:
 - HDTV
 - Washing Machines
 - Microwave
 - Controllers for other household devices such as A/C
 - Digital watches
 - MP3 players
- Not-so-obvious examples:
 - Automobiles
 - Avionics / Flight control
 - Nuclear Power Plants
 - Medical devices

In-Depth Example: Mobile phones

- Multiprocessor
 - 8-bit/32-bit for UI
 - DSP for signals
 - 32-bit in IR port
 - 32-bit in Bluetooth
- 8-100 MB of memory
- All custom chips
- Power consumption & battery life depends on software



But ...

- Dual-core A5 chip
 - package on package (PoP) system-on-a-chip (SoC)
 - 45 nm Dual core GPU PowerVR SGX543MP2 clocked at 200 MHz
- 8MP camera and optics
- IOS 5 and iCloud
- Siri



In-Depth Example: Cars

- Multiple processors
 - Upto100
 - Networked
- Multiple networks
 - Body
 - Engine
 - Telematics
 - Media
 - Safety



Cars

- Function diversity
 - ABS: Anti-lock braking systems
 - Airbags
 - Efficient automatic gearboxes
 - Theft prevention with smart keys
 - Blind-angle alert systems
- Device diversity
 - 8-bit – door locks, lights, etc.
 - 16-bit – most functions
 - 32-bit – engine control, airbags

Little-Known Facts about Cars

- Car electronics is an increasingly important market, requiring new design flows
 - Software is important for value addition
- Comments by major manufacturers
 - Daimler Chrysler: More than 90% of the innovation is from the car electronics (and not from the mechanical parts!)
 - BMW: More than 30% of the manufacturing cost of a car is from the electronic components !
- Reliable/robust ES design flows needed !

Hardware Description Language

This Lecture - HDL

- What and why HDL
- Verilog HDL
- Modelling a simple circuit.
 - Delays
 - Stimulus
- Abstraction Levels
 - Gates
 - Dataflow
 - Procedural

Hardware Description Language (HDL)

- Basic idea is a programming language to describe hardware
- Initial purpose was to allow abstract design and simulation
 - Design could be verified then implemented in hardware
- Now Synthesis tools allow direct implementation from HDL code.
 - Large improvement in designer productivity

HDL

- HDL allows write-run-debug cycle for hardware development.
 - Similar to programming software
 - Much, much faster than design-implement-debug
- Combined with modern Field Programmable Gate Array chips large complex circuits (100000s of gates) can be implemented.

HDLs

- There are many different HDLs
 - Verilog HDL
 - ABEL
 - VHDL
- Verilog is the most common in US industry
- VHDL is the most common in Europe
 - Large standard developed by US DoD
 - VHDL = VHSIC HDL
 - VHSIC = Very High Speed Integrated Circuit

Verilog HDL

- Verilog HDL is the most common in IC industry
 - Easier to use in many ways = better for teaching
 - C - like syntax
- History
 - Developed as proprietry language in 1985
 - Opened as public domain spec in 1990
 - Due to losing market share to VHDL
 - Became IEEE standard in 1995

Verilog HDL

- Verilog constructs are use defined *keywords*
 - Examples: and, or, wire, input output
- One important construct is the *module*
 - Modules have inputs and outputs
 - Modules can be built up of Verilog primitives or of user defined submodules.

Example: Simple Circuit Diagram

 


Fig. 3-37 Circuit to Demonstrate HDL

All examples and code from Mano "Digital Design" 3rd Ed.

Example: Simple Circuit HDL

```
module smpl_circuit(A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    wire e;  
    and g1(e,A,B);  
    not g2(y, C);  
    or g3(x,e,y);  
endmodule
```

- The module starts with **module** keyword and finishes with **endmodule**.
- Internal signals are named with **wire**.
- Comments follow //
- **input** and **output** are ports. These are placed at the start of the module definition.
- Each statement ends with a semicolon, except **endmodule**.

Circuit to code

 


Fig. 3-37 Circuit to Demonstrate HDL

```
module simpl_circuit(A,B,C,x,y);  
  input A,B,C;  
  output x,y;  
  wire e;  
  and g1(e,A,B);  
  not g2(y, C);  
  or g3(x,e,y);  
endmodule
```

Adding Delays

- To simulate a circuits real world behaviour it is important that propogation delays are included.
- The units of time for the simulation can be specified with **timescale**.
 - Default is 1ns with precision of 100ps
- Component delays are specified as #(delay)

Simple Circuit with Delay

```
module circuit_with_delay (A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    wire e;  
    and #(30) g1(e,A,B);  
    or #(20) g3(x,e,y);  
    not #(10) g2(y,C);  
endmodule
```

Input signals

- In order to simulate a circuit the input signals need to be known so as to generate an output signal.
- The input signals are often called the circuit *stimulus*.
- An HDL module is written to provide the circuit stimulus. This is known as a *testbench*.

Testbench

- The *testbench* module includes the module to be tested.
- There are no input or output ports for the testbench.
- The inputs to the test circuit are defined with **reg** and the outputs with **wire**.
- The input values are specified with the keyword **initial**
- A sequence of values can be specified between **begin** and **end**.

Signal Notation

- In Verilog signals are generalised to support multi-bit values (e.g. for buses)

- The notation

$$A = 1'b0;$$

- means signal A is one bit with value zero.

- The end of the simulation is specified with **\$finish.**

Stimulus module for simple circuit

```
module stimcrct;
  reg A,B,C;
  wire x,y;
  circuit_with_delay cwd(A,B,C,x,y);
  initial
    begin
      A = 1'b0; B = 1'b0; C = 1'b0;
      #100
      A = 1'b1; B = 1'b1; C = 1'b1;
      #100 $finish;
    end
endmodule
```

Timing Diagram

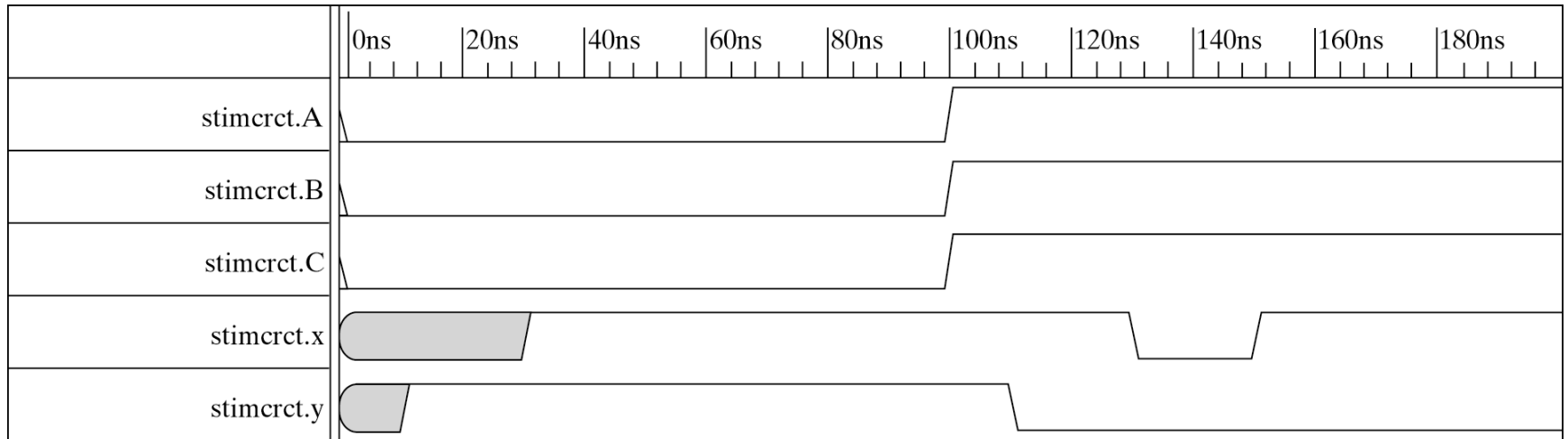


Fig. 3-38 Simulation Output of HDL Example 3-3

Gate Level Modelling

- The simple circuit used so far is an example of *gate-level modelling*.
- The module is a text description of the circuit layout.
- Verilog has all the standard gates
 - `and`, `nand`
 - `or`, `nor`
 - `xor`, `xnor`
 - `not`, `buf`

Dataflow modelling

- Another level of abstraction is to model dataflow.
- In dataflow models, signals are continuously assigned values using the **assign** keyword.
- **assign** can be used with Boolean expressions.
 - Verilog uses & (and), | (or), ^ (xor) and ~ (not)
- Logic expressions and binary arithmetic are also possible.

Simple Circuit Boolean Expression

 


Fig. 3-37 Circuit to Demonstrate HDL

```
//Circuit specified with Boolean equations
module circuit_bln (x,y,A,B,C);
    input A,B,C;
    output x,y;
    assign x = A | (B & ~C);
    assign y = ~C ;
endmodule
```

Behavioural Modelling

- Represents circuits at functional and algorithmic level.
- Use procedural statements similar in concept to procedural programming languages (e.g. C, Java),
- Behavioural modelling is mostly used to represent sequential circuits.

Behavioural Modelling

- Behavioural models place procedural statements in a block after the **always** keyword.
- The **always** keyword takes a list of variables. The block of statements is executed whenever one of the variables changes.
- The target variables are of type **reg**. This type retains its value until a new value is assigned.

Behavioral description of 2-input mux

```
module mux2x1_bh(A, B, select, OUT);  
    input A, B, select;  
    output OUT;  
    reg OUT;  
    always @ (select or A or B)  
        if (select == 1) OUT = A;  
        else OUT = B;  
  
endmodule
```


HDL Summary

- Hardware Description Languages allow fast design and verification of digital circuits.
- Accurate simulation and testing requires delays and inputs to be specified.
- There are three different levels of abstraction for modelling circuits.

Why This Course?

- Because it is FUN intellectually!
- Because HDL prog. become increasingly more critical



Aerospace/Defense



Industrial/Scientific/Medi
cal



Broadcast



Wired communication



Consumer



Wireless communication



HPC and storage



Automobile

Class goal

- Learn about basic concept and techniques of hardware/software co-design, ...
- Hands-on class projects
 - Complete FPGA design flow to implement a “real” embedded computing system
 - Improve your HDL programming skills
 - Improve your Software programming skill
 - Learning by doing

Administrative issues

- Fill out the student info sheet
 - Name, status, reason of taking this class, expectations, prior knowledge, ...
- Pre-requisites
 - EEL 3342: Digital Logic Design
 - Course self-contained, but logic design and computer architecture knowledge helpful (EEL 4768: Computer Architecture)
 - Willingness to work hard
- Information distribution
 - Webpage: www.eecs.ucf.edu/~mingjie/EEL4783_2012/index.html

Lecture schedule

See Webpage:

www.eecs.ucf.edu/~mingjie/EEL4783_2012

Final issues

- Please fill out the student info sheet before leaving
- Come by my office hours (right after class)
- Any questions or concerns?