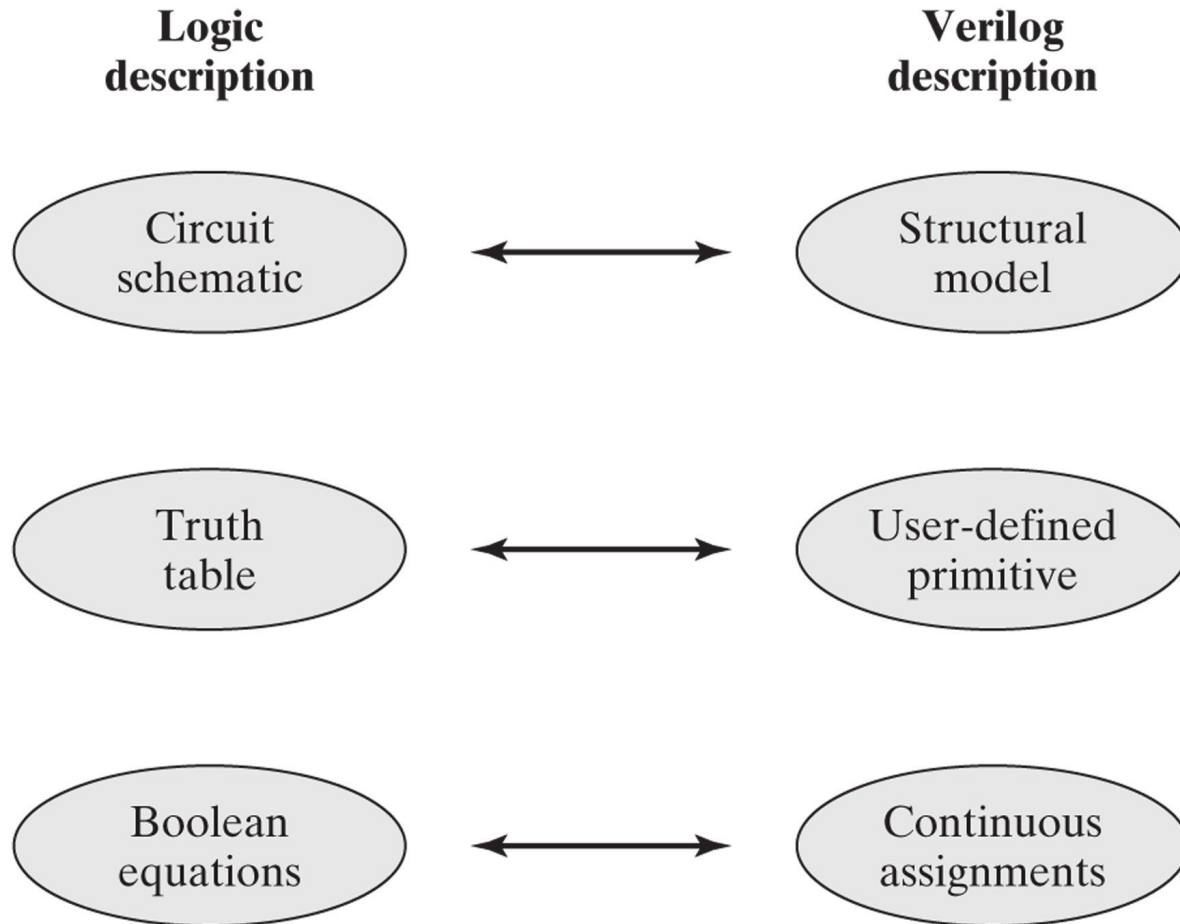

EEL 4783: HDL in Digital System Design

Lecture 3: Logic Design with Behavioral Models


Prof. Mingjie Lin



HDL Levels



An AOI Circuit

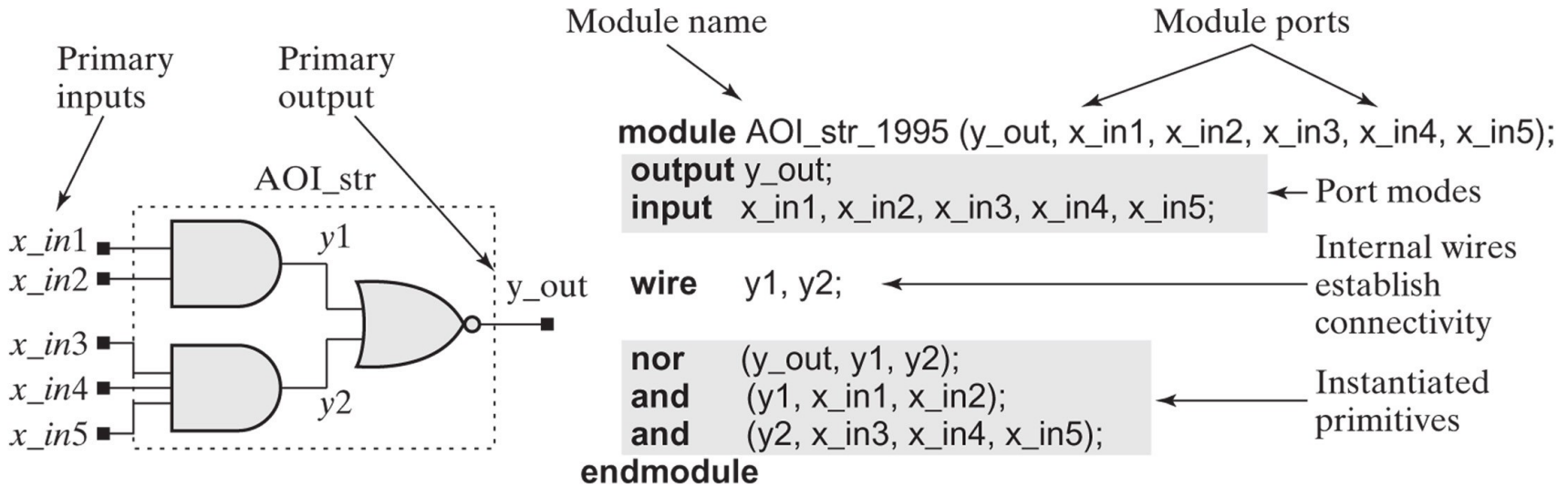

(a)

```

module AOI_str_2005 (output  $y_{out}$ , input  $x_{in1}$ ,  $x_{in2}$ ,  $x_{in3}$ ,  $x_{in4}$ ,  $x_{in5}$ );
wire  $y1$ ,  $y2$ ;

nor ( $y_{out}$ ,  $y1$ ,  $y2$ );
and ( $y1$ ,  $x_{in1}$ ,  $x_{in2}$ );
and ( $y2$ ,  $x_{in3}$ ,  $x_{in4}$ ,  $x_{in5}$ );
endmodule


```

(b)

Behavior Descriptions


```
module AOI_5_CA0 (y_out, x_in1, x_in2, x_in3, x_in4, x_in5);  
  input          x_in1, x_in2, x_in3, x_in4, x_in5;  
  output        y_out;  
  
  assign y_out = ~((x_in1 & x_in2) | (x_in3 & x_in4 & x_in5));  
  
endmodule
```

Modified AOI

 

```
module AOI_5_CA2 (y_out, x_in1, x_in2, x_in3, x_in4, x_in5, enable);  
  input          x_in1, x_in2, x_in3, x_in4, x_in5, enable;  
  output         y_out;  
  
  wire y_out = enable ? ~((x_in1 & x_in2) |(x_in3 & x_in4 & x_in5)) : 1'bz;  
  
endmodule
```

32-Bit Two-Channel MUX

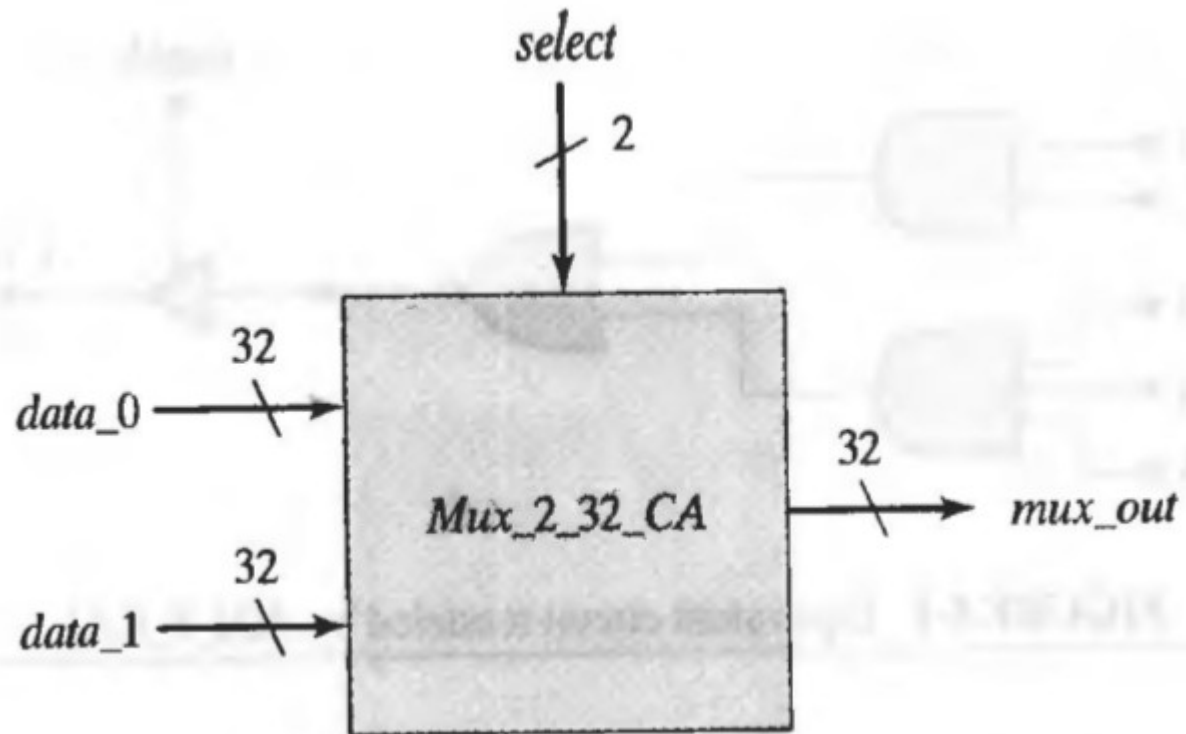

32-Bit Two-Channel MUX

```
module Mux_2_32_CA ( mux_out, data_1, data_0, select);  
  parameter word_size = 32;  
  output [word_size - 1: 0] mux_out;  
  input [word_size - 1: 0] data_1, data_0;  
  input select;  
  
  assign mux_out = select ? data_1 : data_0;  
endmodule
```

Propagation Delay

```
module AOI_5_CA3 (y_out, x_in1, x_in2, x_in3, x_in4);  
  input          x_in1, x_in2, x_in3, x_in4;  
  output        y_out;  
  
  wire #1 y1 = x_in1 & x_in2;          // Bitwise and operation  
  wire #1 y2 = x_in3 & x_in_4;  
  wire #1 y_out = ~(y1 | y2);         // Complement the result of bitwise OR operation  
endmodule
```

 

Continuous Assignments

```
module compare_2_CA0 (A_lt_B, A_gt_B, A_eq_B, A1, A0, B1, B0);  
  input  A1, A0, B1, B0;  
  output A_lt_B, A_gt_B, A_eq_B;  
  
  assign A_lt_B = (~A1) & B1 | (~A1) & (~A0) & B0 | (~A0) & B1 & B0;  
  
  assign A_gt_B = A1 & (~B1) | A0 & (~B1) & (~B0) | A1 & A0 & (~B0);  
  
  assign A_eq_B = (~A1) & (~A0) & (~B1) & (~B0) | (~A1) & A0 & (~B1) & B0  
    | A1 & A0 & B1 & B0 | A1 & (~A0) & B1 & (~B0);  
  
endmodule
```

Latches and Level-Sensitive Circuits


```
assign q = set ~& qbar;  
assign qbar = rst ~& q;
```

```
module Latch_CA (q_out, data_in, enable);  
output q_out;  
input data_in, enable;  
  
assign q_out = enable ? data_in : q_out;  
endmodule
```



More Complex Latch
 
```
module Latch_Rbar_CA (q_out, data_in, enable, reset);  
    output          q_out;  
    input           data_in, enable, reset;  
  
    assign q_out = !reset ? 0 : enable ? data_in : q_out;  
endmodule
```



Cyclic Behavior of Flip-Flops

```
module df_behav (q, q_bar, data, set, reset, clk);  
  input          data, set, clk, reset;  
  output        q, q_bar;  
  reg           q;  
  
  assign q_bar = ~ q;  
  
  always @ (posedge clk) // Flip-flop with synchronous set/reset  
  
  begin  
    if (reset == 0) q <= 0;  
    else if (set == 0) q <= 1;  
    else q <= data;  
  end  
endmodule
```

Even More Complex FFs

```
module asynch_df_behav (q, q_bar, data, set, clk, reset );  
  input          data, set, reset, clk;  
  output        q, q_bar;  
  reg           q;  
  
  assign        q_bar = ~q;  
  
  always @ (negedge set or negedge reset or posedge clk)  
  begin  
    if (reset == 0) q <= 0;  
    else if (set == 0) q <= 1;  
    else q <= data;           // synchronized activity  
  end  
endmodule
```

Latch vs. Flip-Flop

```
module tr_latch (q_out, enable, data);
  output q_out;
  input enable, data;
  reg q_out;

  always @ (enable or data)
    begin
      if (enable) q_out = data;
    end
endmodule
```

```
module df_behav (q, q_bar, data, set, reset, clk);
  input data, set, clk, reset;
  output q, q_bar;
  reg q;

  assign q_bar = ~ q;

  always @ (posedge clk) // Flip-flop with synchronous set/reset
    begin
      if (reset == 0) q <= 0;
      else if (set == 0) q <= 1;
      else q <= data;
    end
endmodule
```

Final issues

- Please fill out the student info sheet before leaving
- Come by my office hours (right after class)
- Any questions or concerns?