

---

# EEL 4783: HDL in Digital System Design

## Lecture 4: Logic Design with Behavioral Models (cont.)

Prof. Mingjie Lin



# Latch vs. Flip-Flop

```
module tr_latch (q_out, enable, data);
  output q_out;
  input enable, data;
  reg q_out;

  always @ (enable or data)
    begin
      if (enable) q_out = data;
    end
endmodule
```

```
module df_behav (q, q_bar, data, set, reset, clk);
  input data, set, clk, reset;
  output q, q_bar;
  reg q;

  assign q_bar = ~ q;

  always @ (posedge clk) // Flip-flop with synchronous set/reset
    begin
      if (reset == 0) q <= 0;
      else if (set == 0) q <= 1;
      else q <= data;
    end
endmodule
```


# Different Styles of Behavioral Modeling

---

- Continuous Assignment Model
- Data-Flow/RTL Model
- Algorithm-Based Model


# Continuous Assignment Models

---

 


```
module compare_2_CA1 (A_lt_B, A_gt_B, A_eq_B, A1, A0, B1, B0);  
  input      A1, A0, B1, B0;  
  output    A_lt_B, A_gt_B, A_eq_B;  
  
  assign    A_lt_B = ({A1,A0} < {B1,B0});  
  assign    A_gt_B = ({A1,A0} > {B1,B0});  
  assign    A_eq_B = ({A1,A0} == {B1,B0});  
endmodule
```

# Continuous Assignment Models

 

```
module compare_32_CA (A_gt_B, A_lt_B, A_eq_B, A, B);  
  parameter    word_size = 32;  
  input        [word_size-1:0] A, B;  
  output       A_gt_B, A_lt_B, A_eq_B;  
  
  assign       A_gt_B = (A > B),           // Note: list of multiple assignments  
                A_lt_B = (A < B),  
                A_eq_B = (A == B);  
  
endmodule
```

# Data-Flow/RTL Models

 


```
module compare_2_RTL (A_lt_B, A_gt_B, A_eq_B, A1, A0, B1, B0);  
  Input      A1, A0, B1, B0;  
  output    A_lt_B, A_gt_B, A_eq_B;  
  reg       A_lt_B, A_gt_B, A_eq_B;  
  
  always @ (A0 or A1 or B0 or B1) begin  
    A_lt_B =  {{A1,A0} < {B1,B0}};  
    A_gt_B =  {{A1,A0} > {B1,B0}};  
    A_eq_B =  {{A1,A0} == {B1,B0}};  
  end  
endmodule
```

# Blocking vs. Non-Blocking Statements

---

- `A=B;`
- `A<=B;`
- `assign A = B;`


# 4-Bit Shift Register

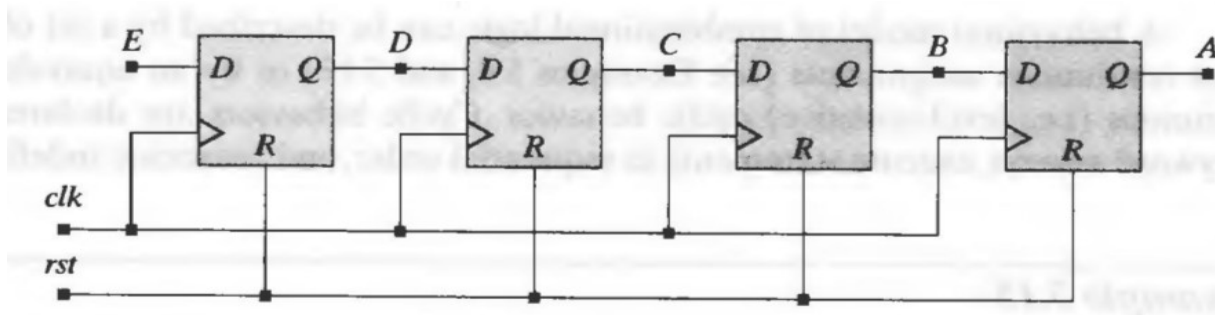

```
module shiftreg_PA (E, A, B, C, D, clk, rst);  
    output A;  
    input E;  
    input clk, rst;  
    reg A, B, C, D;  
  
    always @ (posedge clk or posedge rst) begin  
        if (reset) begin A = 0; B = 0; C = 0; D = 0; end  
        else begin  
            A = B;  
            B = C;  
            C = D;  
            D = E;  
        end  
    end  
end  
endmodule
```



# 4-Bit Shift Register

 

```
module shiftreg_nb (A, E, clk, rst);
    output A;
    input E;
    input clk, rst;
    reg A, B, C, D;

    always @ (posedge clk or posedge rst) begin
        if (rst) begin A <= 0; B <= 0; C <= 0; D <= 0; end
        else begin
            A <= B;           // D <= E;
            B <= C;           // C <= D;
            C <= D;           // B <= D;
            D <= E;           // A <= B;
        end
    end
endmodule
```

# Algorithm-Based Model

```
module compare_2_algo (A_lt_B, A_gt_B, A_eq_B, A, B);  
  output      A_lt_B, A_gt_B, A_eq_B;  
  input [1: 0]  A, B;  
  
  reg         A_lt_B, A_gt_B, A_eq_B;  
  
  always @ (A or B)    // Level-sensitive behavior  
  begin  
    A_lt_B = 0;  
    A_gt_B = 0;  
    A_eq_B = 0;  
    if (A == B)        A_eq_B = 1;    // Note: parentheses are required  
    else if (A > B)    A_gt_B = 1;  
    else               A_lt_B = 1;  
  end  
endmodule
```


# Behavior Models of MUX

```
module Mux_4_32_case
  (mux_out, data_3, data_2, data_1, data_0, select, enable);
  output [31: 0] mux_out;
  input [31: 0] data_3, data_2, data_1, data_0;
  input [1: 0] select;

  input enable;
  reg [31: 0] mux_int;

  assign mux_out = enable ? mux_int : 32'bz;

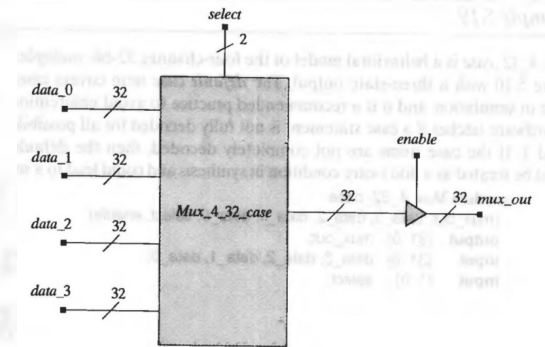  always @ ( data_3 or data_2 or data_1 or data_0 or select)
    case (select)
      0: mux_int = data_0;
      1: mux_int = data_1;
      2: mux_int = data_2;
      3: mux_int = data_3;
      default: mux_int = 32'bx;
    endcase
  endmodule
```



# Behavior Models of MUX (cont.)

---

```
module Mux_4_32_if
  (mux_out, data_3, data_2, data_1, data_0, select, enable);
output [31: 0] mux_out;
input  [31: 0] data_3, data_2, data_1, data_0;
input  [1: 0]  select;
input          enable;
reg    [31: 0] mux_int;

assign mux_out = enable ? mux_int : 32'bz;



always @ ( data_3 or data_2 or data_1 or data_0 or select)
  if (select == 0) mux_int = data_0; else
    if (select == 1) mux_int = data_1; else
      if (select == 2) mux_int = data_2; else
        if (select == 3) mux_int = data_3; else mux_int = 32'bx;
endmodule
```

# Behavior Models of MUX (cont.)

---

```
module Mux_4_32_CA (mux_out, data_3, data_2, data_1, data_0, select, enable);  
  output [31: 0] mux_out;  
  input  [31: 0] data_3, data_2, data_1, data_0;  
  input  [1: 0]  select;  
  input           enable;  
  wire   [31: 0] mux_int;  
  assign mux_out = enable ? mux_int : 32'bz;  
  assign mux_int = (select == 0) ? data_0 :  
                   (select == 1) ? data_1 :  
                   (select == 2) ? data_2 :  
                   (select == 3) ? data_3 : 32'bx;  
endmodule
```

# Encoder

  



# Encoder

---

```
module encoder (Code, Data);  
  output      [2: 0] Code;  
  input       [7: 0] Data;  
  reg         [2: 0] Code;  
  
  always @ (Data)  
  begin  
    if (Data == 8'b00000001) Code = 0; else  
    if (Data == 8'b00000010) Code = 1; else  
    if (Data == 8'b00000100) Code = 2; else  
    if (Data == 8'b00001000) Code = 3; else  
    if (Data == 8'b00010000) Code = 4; else  
    if (Data == 8'b00100000) Code = 5; else  
    if (Data == 8'b01000000) Code = 6; else  
    if (Data == 8'b10000000) Code = 7; else Code = 3'bx;  
  end
```

---

# Encoder

---

```
always @ (Data)  
  case (Data)  
    8'b00000001 : Code = 0;  
    8'b00000010 : Code = 1;  
    8'b00000100 : Code = 2;  
    8'b00001000 : Code = 3;  
    8'b00010000 : Code = 4;  
    8'b00100000 : Code = 5;  
    8'b01000000 : Code = 6;  
    8'b10000000 : Code = 7;  
    default      : Code = 3'bx;  
  endcase  
*/  
endmodule
```



# Final issues

---

- Please fill out the student info sheet before leaving
- Come by my office hours (right after class)
- Any questions or concerns?