
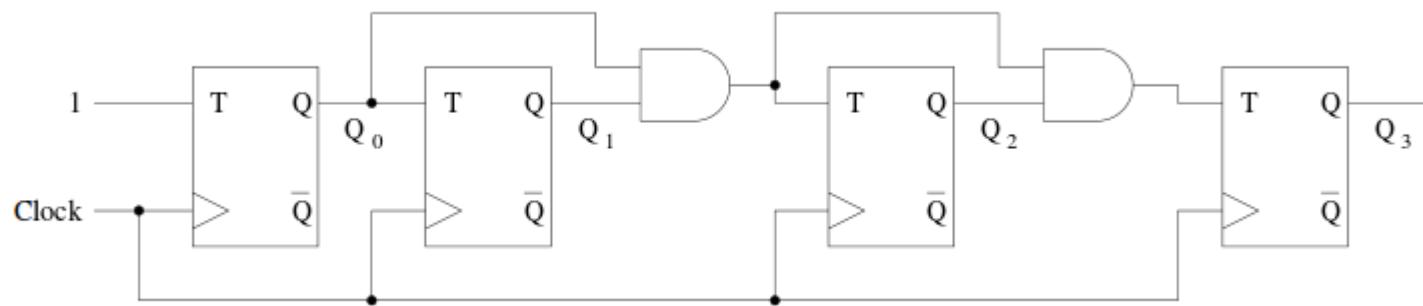


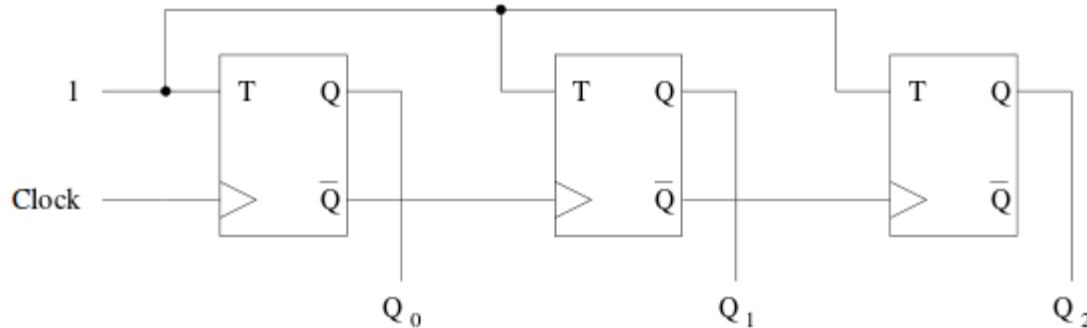

UCF

Stands For Opportunity

Example: 4-Bit Ripple Adder



Example: 4-Bit Ripple Adder

```
// module D_FF with synchronous reset
module D_FF(q, d, clk, reset);

output q;
input d, clk, reset;
reg q;

// Lots of new constructs. Ignore the functionality of the
// constructs.
// Concentrate on how the design block is built in a top-down fashion.
always @(posedge reset or negedge clk)
if (reset)
    q <= 1'b0;
else
    q <= d;

endmodule
```

Example: 4-Bit Ripple Adder

```
module T_FF(q, clk, reset);  
  
output q;  
input clk, reset;  
wire d;  
  
D_FFdff0(q, d, clk, reset);  
not n1(d, q); // not is a Verilog-provided primitive. case sensitive  
endmodule
```

```
module stimulus;

reg clk;
reg reset;
wire[3:0] q;

// instantiate the design block
ripple_carry_counter r1(q, clk, reset);

// Control the clk signal that drives the design block. Cycle time = 10
initial
    clk = 1'b0; //set clk to 0
always
    #5 clk = ~clk; //toggle clk every 5 time units

// Control the reset signal that drives the design block
// reset is asserted from 0 to 20 and from 200 to 220.
initial
begin
    reset = 1'b1;
    #15 reset = 1'b0;
    #180 reset = 1'b1;
```


Example: 4-Bit Ripple Adder

```
#10 reset = 1'b0;  
#20 $finish; //terminate the simulation  
end  
  
// Monitor the outputs  
initial  
    $monitor($time, " Output q = %d", q);  
  
endmodule
```

Example: 4-Bit Ripple Adder

```
module ripple_carry_counter(q, clk, reset);  
  
output [3:0] q;  
input clk, reset;  
  
//4 instances of the module T_FF are created.  
T_FF tff0(q[0],clk, reset);  
T_FF tff1(q[1],q[0], reset);  
T_FF tff2(q[2],q[1], reset);  
T_FF tff3(q[3],q[2], reset);  
  
endmodule
```

LFSR-Linear-Feedback Shift Register

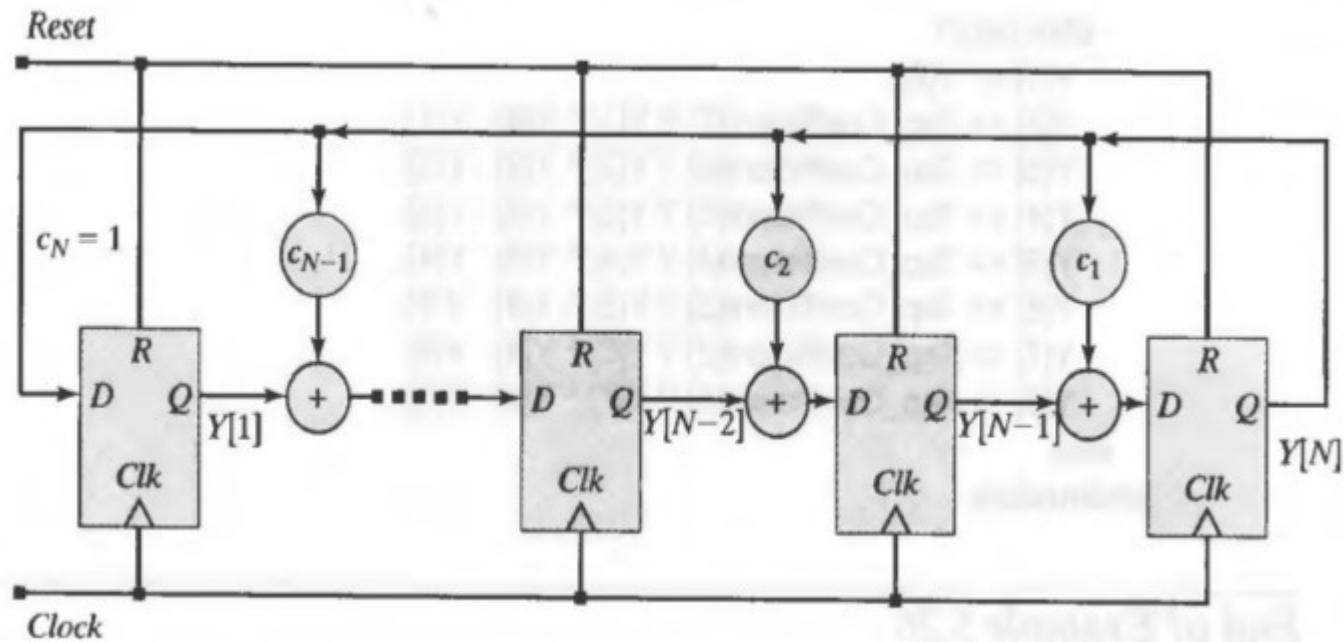

Data-Flow Model of LFSR


```
module Auto_LFSR_RTL (Y, Clock, Reset);
parameter Length = 8;
parameter initial_state = 8'b1001_0001; // 91h
parameter [1: Length] Tap_Coefficient = 8'b1100_1111;

input Clock, Reset;
output [1: Length] Y;
reg [1: Length] Y;

always @ (posedge Clock)
if (Reset == 0) Y <= initial_state; // Active-low reset to initial state

else begin
    Y[1] <= Y[8];
    Y[2] <= Tap_Coefficient[7] ? Y[1] ^ Y[8] : Y[1];
    Y[3] <= Tap_Coefficient[6] ? Y[2] ^ Y[8] : Y[2];
    Y[4] <= Tap_Coefficient[5] ? Y[3] ^ Y[8] : Y[3];
    Y[5] <= Tap_Coefficient[4] ? Y[4] ^ Y[8] : Y[4];
    Y[6] <= Tap_Coefficient[3] ? Y[5] ^ Y[8] : Y[5];
    Y[7] <= Tap_Coefficient[2] ? Y[6] ^ Y[8] : Y[6];
    Y[8] <= Tap_Coefficient[1] ? Y[7] ^ Y[8] : Y[7];
end
endmodule
```

Repetitive Logic Modeling

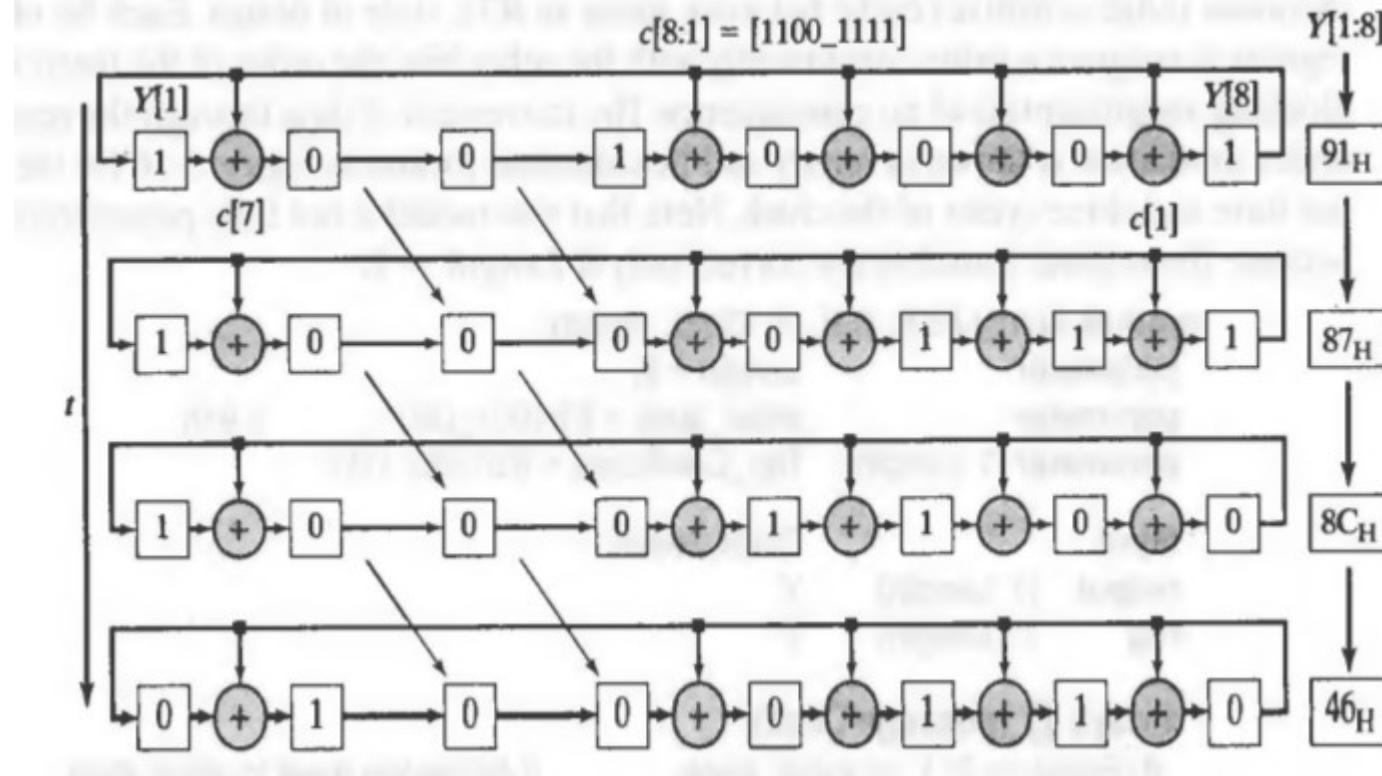

Repetitive Logic Modeling

```
module Auto_LFSR_ALGO (Y, Clock, Reset);
parameter Length = 8;
parameter initial_state = 8'b1001_0001;
parameter [1: Length] Tap_Coefficient = 8'b1100_1111;
input Clock, Reset;
output [1: Length] Y;
integer Cell_ptr;
reg Y;

always @ (posedge Clock)
begin
if (Reset == 0) Y <= initial_state; // Arbitrary initial state, 91h
else begin for (Cell_ptr = 2; Cell_ptr <=Length; Cell_ptr = Cell_ptr +1)
if (Tap_Coefficient [Length - Cell_ptr + 1] == 1)
Y[Cell_ptr] <= Y[Cell_ptr - 1]^ Y [Length];
else
Y[Cell_ptr] <= Y[Cell_ptr - 1];
Y[1] <= Y[Length];
end
end
endmodule
```

A for loop has the form:

```
for(initial_statement; control_expression; index_statement)
statement_for_execution;
```

For loop, repeat loop, while loop, ...

```
for(initial_statement; control_expression; index_statement)  
statement_for_execution;
```

```
...  
word_address = 0;  
repeat (memory_size)  
begin  
    memory [ word_address] = 0;  
    word_address = word_address + 1;  
end  
...
```

```
while (expression) statement;
```

Majority Module

```
module Majority_4b (Y, A, B, C, D);
  input  A, B, C, D;
  output Y;
  reg   Y;
  always @ (A or B or C or D) begin
    case ({A, B,C, D})
      7, 11, 13, 14, 15:  Y = 1;
      default           Y = 0;
    endcase
  end
endmodule
```

```
module Majority (Y, Data);
  parameter size = 8;
  parameter max = 3;
```

```
parameter majority = 5;
input   [size-1: 0] Data;
output  Y;
reg    [max-1: 0] count;
integer k;

always @ (Data) begin
  count = 0;
  for (k = 0; k < size; k = k + 1) begin
    if (Data[k] == 1) count = count + 1;
  end
  Y = (count >= majority);
end
endmodule
```

Parametrized Models

```
module Auto_LFSR_Param (Y, Clock, Reset);
    parameter Length = 8;
    parameter initial_state = 8'b1001_0001; //      Arbitrary initial state
    parameter [1: Length] Tap_Coefficient = 8'b1100_1111;

    input Clock, Reset;
    output [1: Length] Y;
    reg [1: Length] Y;
    integer k;

    always @ (posedge Clock)
        if (Reset==0) Y <= initial_state;
        else begin
            for (k = 2; k <= Length; k = k + 1)
                Y[k] <= Tap_Coefficient[Length-k+1] ? Y[k-1] ^ Y[Length] : Y[k-1];
            Y[1] <= Y[Length];
        end
    endmodule
```

Clock Signal Generation

```
parameter half_cycle = 50;
parameter stop_time = 350;
initial
begin: clock_loop      // Note: clock_loop is a named block of statements
  clock = 0;
  forever
    begin
      #half_cycle clock = 1;
      #half_cycle clock = 0;
    end
  end
initial
#350 disable clock_loop;
```

Finding First 1 Circuit

```
module find_first_one(index_value, A_word, trigger);
    output [3: 0] index_value;
    input [15: 0] A_word;
    input          trigger;
    reg   [3: 0]   index_value;
    always @ (trigger)
        begin: search_for_1
            index_value = 0;
            for (index_value = 0; index_value <= 15; index_value = index_value + 1)
                if (A_word[index_value] == 1) disable search_for_1;
            end
        endmodule
```

Final issues

- Please fill out the student info sheet before leaving
- Come by my office hours (right after class)
- Any questions or concerns?