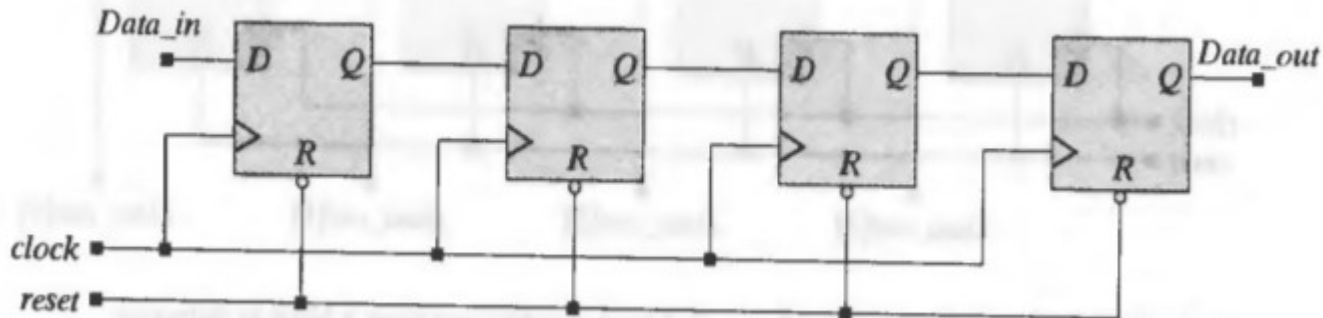

EEL 4783: HDL in Digital System Design

Lecture 6: Verilog Examples

Prof. Mingjie Lin




Shift Register



```
module Shift_reg4 (Data_out, Data_in, clock, reset);  
    output        Data_out;  
    input         Data_in, clock, reset;  
    reg [3: 0]   Data_reg;  
  
    assign        Data_out = Data_reg[0];  
    always @ (negedge reset or posedge clock)  
    begin  
        if (reset == 1'b0)    Data_reg <= 4'b0;  
        else                   Data_reg <= {Data_in, Data_reg[3:1]};  
    end  
endmodule
```


SR with Parallel Loads

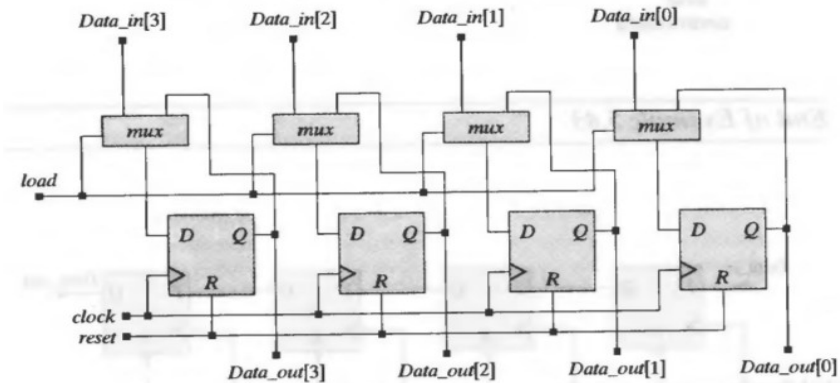


```
module Par_load_reg4 (Data_out, Data_in, load, clock, reset);
  input      [3: 0]  Data_in;
  input      load, clock, reset;
  output     [3: 0]  Data_out;           // Port size
  reg        Data_out;                   // Data type

  always @ (posedge reset or posedge clock)
  begin
    if (reset == 1'b1)
      Data_out <= 4'b0;
    else if (load == 1'b1)
      Data_out <= Data_in;
  end
endmodule
```

Barrel SR

 

(a)

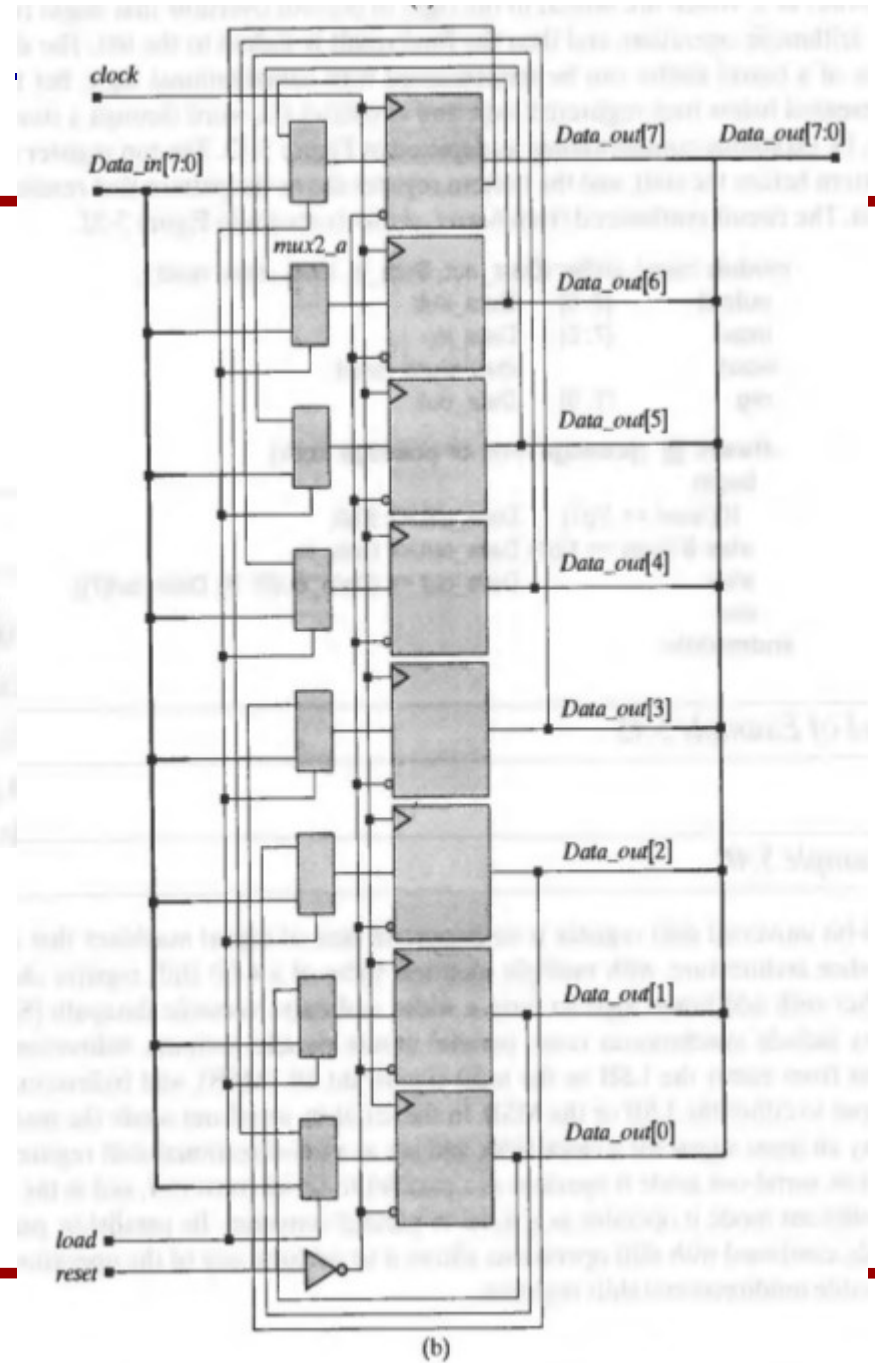

(b)

Barrel SR


```
module barrel_shifter (Data_out, Data_in, load, clock, reset);
  output [7: 0] Data_out;
  input [7: 0] Data_in;
  input load, clock, reset;
  reg [7: 0] Data_out;

  always @ (posedge reset or posedge clock)
  begin
    if (reset == 1'b1) Data_out <= 8'b0;
    else if (load == 1'b1) Data_out <= Data_in;
    else Data_out <= {Data_out[6: 0], Data_out[7]};
  end
endmodule
```

Universal RF

```
module Universal_Shift_Reg (Data_Out, MSB_Out, LSB_Out, Data_In,  
    MSB_In, LSB_In, s1, s0, clk, rst);  
    output [3: 0] Data_Out;  
    output      MSB_Out, LSB_Out;  
    input  [3: 0] Data_In;  
    input      MSB_In, LSB_In;  
    input      s1, s0, clk, rst;  
    reg      Data_Out;  
  
    assign MSB_Out = Data_Out[3];  
    assign LSB_Out = Data_Out[0];  
  
    always @ (posedge clk) begin  
        if (rst) Data_Out <= 0;  
        else case ({s1, s0})  
            0: Data_Out <= Data_Out;           // Hold  
            1: Data_Out <= {MSB_In, Data_Out[3:1]}; // Serial shift from MSB  
            2: Data_Out <= {Data_Out[2: 0], LSB_In}; // Serial shift from LSB  
            3: Data_Out <= Data_In;           // Parallel Load  
        endcase  
    end  
endmodule
```

Bi-Directional Bus

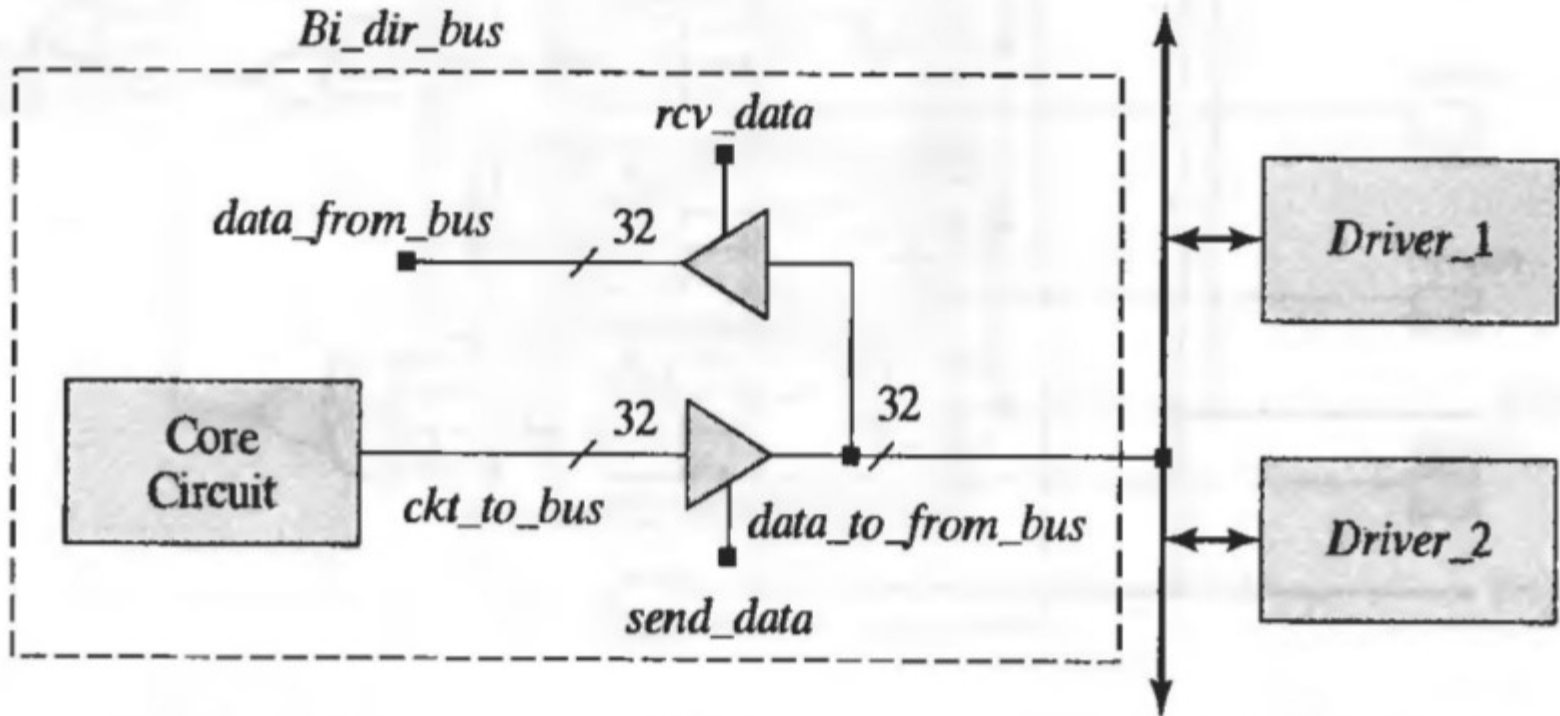

Bi-Directional Bus

```
module Bi_dir_bus (data_to_from_bus, send_data, rcv_data);  
  inout [31: 0] data_to_from_bus;  
  input         send_data, rcv_data;  
  wire [31: 0] ckt_to_bus;  
  wire [31: 0] data_to_from_bus, data_from_bus;  
  
  assign data_from_bus = (rcv_data) ? data_to_from_bus : 32'bz;  
  assign data_to_from_bus = (send_data) ? reg_to_bus : data_to_from_bus;  
  
  // Behavior using data_from_bus and generating  
  // ckt_to_bus goes here  
  
endmodule
```


When a FF is created?

Synthesis Tip

A variable that is referenced within an edge-sensitive behavior before it is assigned value in the behavior will be synthesized as the output of a flip-flop.


Sync. Data Swapping

```
module swap_synch (data_a, data_b set1, set2, clk,);  
  output          data_a, data_b;  
  input           clk, set1, set2, swap;  
  reg             data_a, data_b;  
  
  always @ (posedge clk)  
  begin  
    if (set1) begin data_a <= 1; data_b <= 0; end else  
      if (set2) begin data_a <= 0; data_b <= 1; end  
      else  
        begin  
          data_b <= data_a;  
          data_a <= data_b;  
        end  
      end  
  
  end  
endmodule
```

Sync. Data Swapping

```
module swap_synch (data_a, data_b set1, set2, clk,);  
output          data_a, data_b;  
input          clk, set1, set2, swap;  
reg           data_a, data_b;  
  
always @ (posedge clk)  
begin  
  if (set1) begin data_a <= 1; data_b <= 0; end else  
    if (set2) begin data_a <= 0; data_b <= 1; end  
    else  
      begin  
        data_b <= data_a;  
        data_a <= data_b;  
      end  
    end  
end  
endmodule
```

Sync. Data Swapping

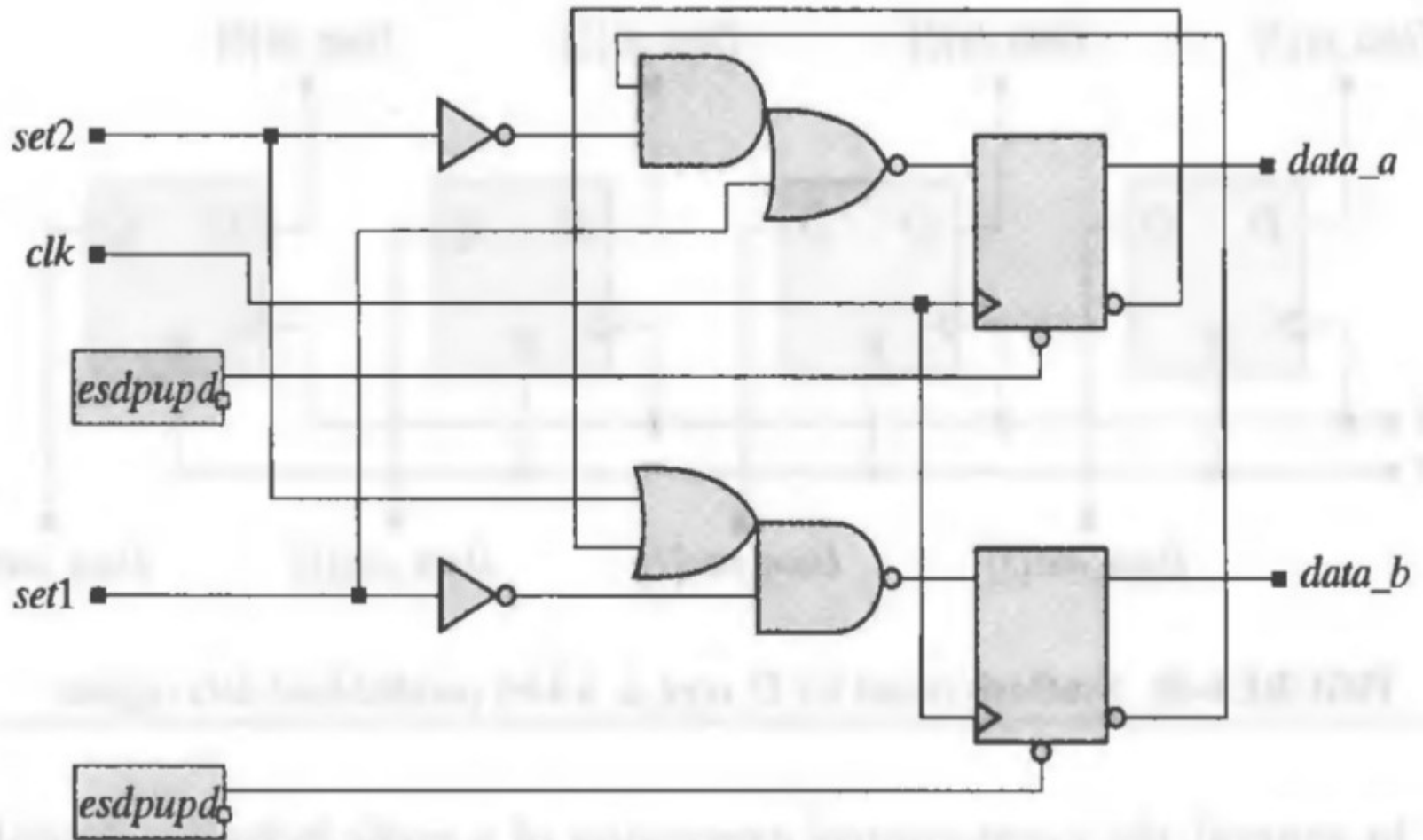

S

S

S

S

S

Final issues

- Please fill out the student info sheet before leaving
- Come by my office hours (right after class)
- Any questions or concerns?