

---

# EEL 4783: HDL in Digital System Design

## Lecture 7: HDL Programming for Logic Synthesis

Prof. Mingjie Lin




# How to Write Synthesis-Friendly HDL Codes?

---


- Detect and eliminate redundant logic?
- Detect combinational feedback loops
- Exploit Don't care conditions
- Detect unused states
- Detect and collapse equivalent states
- Synthesize optimized logic circuits

# Behavioral, Structural, Physical Views

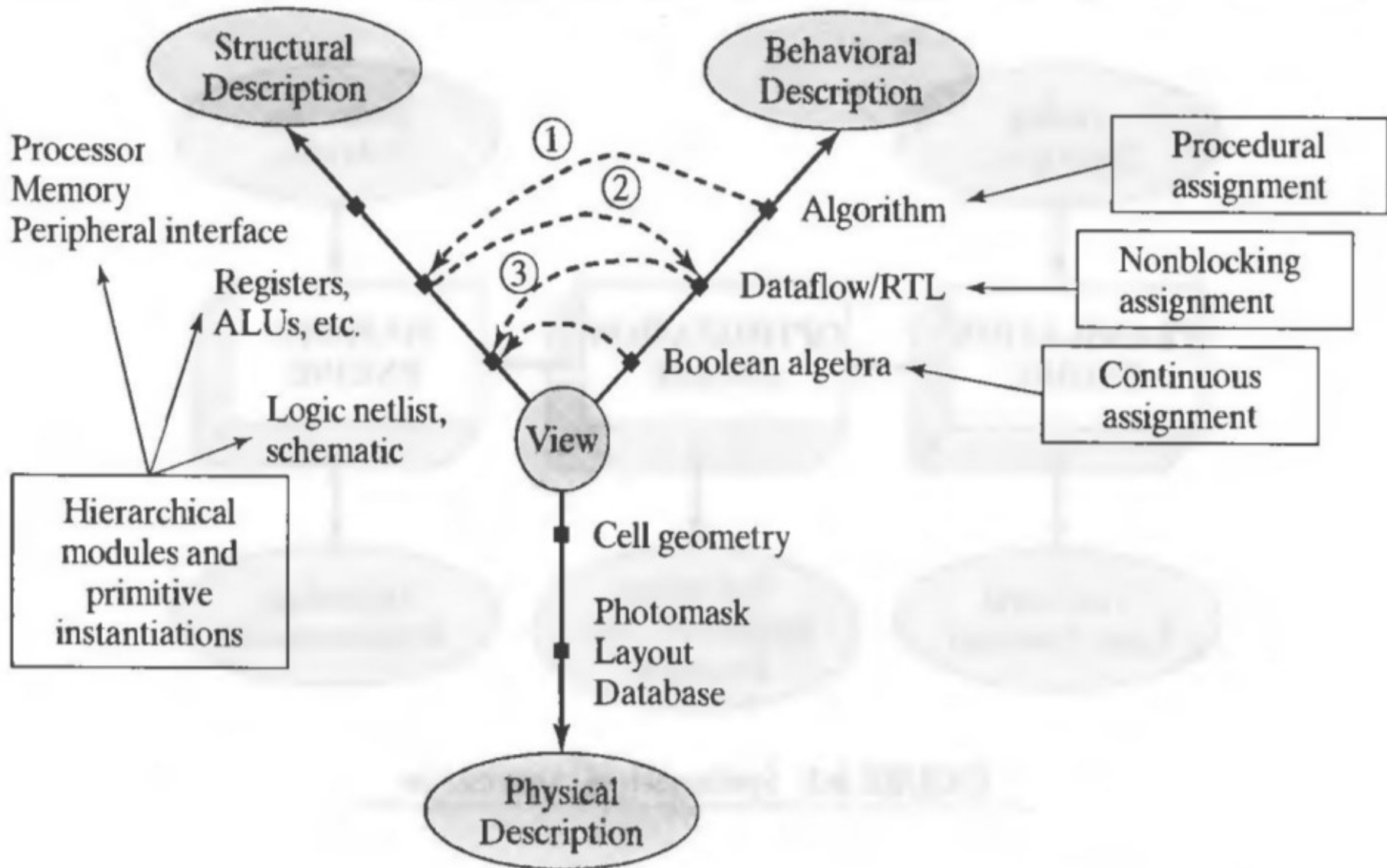


# Synthesis Tools Organization

---

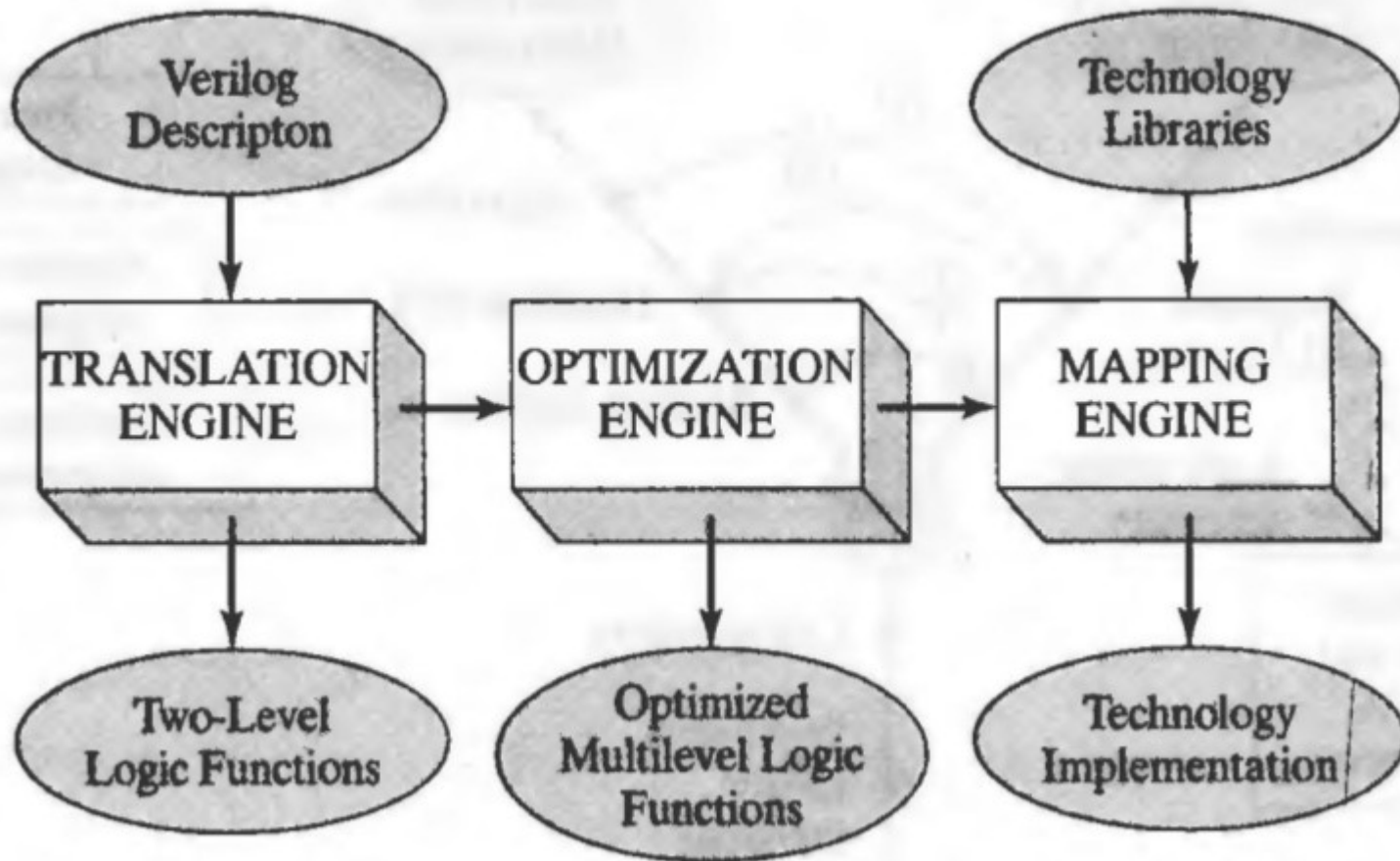


# Sum-of-Products Implementations

$$F = abc + abd + a'b'c' + b'c'd'$$


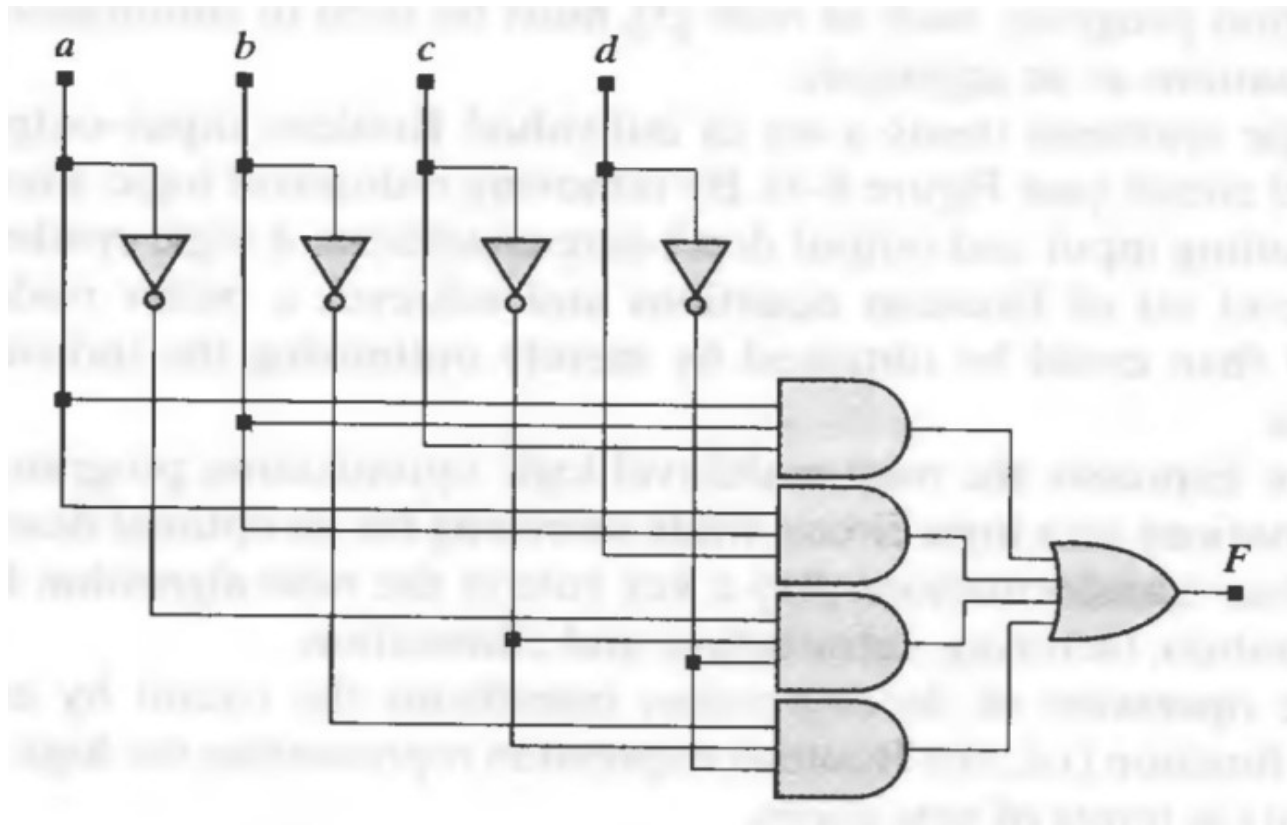

 
# Optimized Design

$$F = XY + X'Y'$$
$$X = ab$$
$$Y = c + d$$




# DAG Graph

  

---


$$F = ac + ad + bc + bd + e$$

 




---



$$F = (a + b)(c + d) + e$$

 


# Logic Optimization

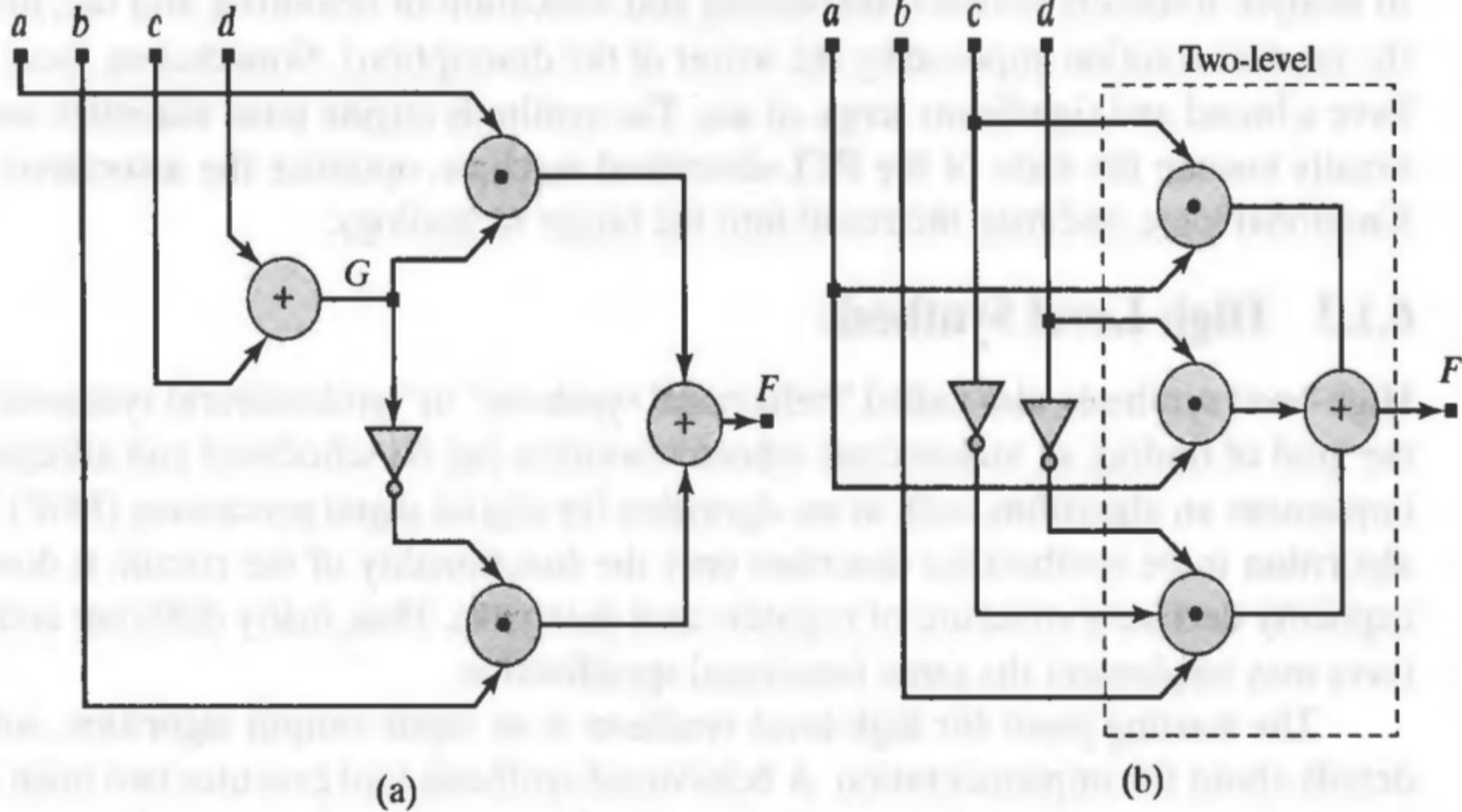

# Synthesis of Comb. Circuits

 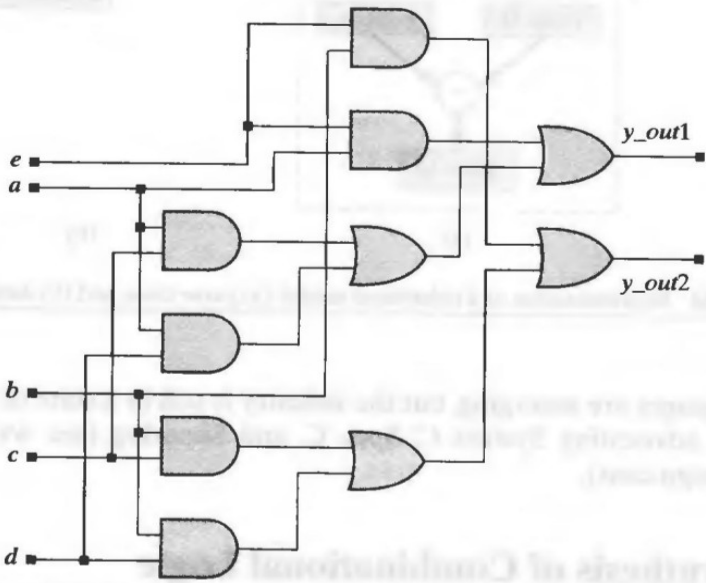
 
```
module boole_opt(y_out1, y_out2, a, b, c, d, e);  
  output y_out1, y_out2;  
  input a, b, c, d, e;  
  
  and (y1, a, c);  
  and (y2, a, d);  
  and (y3, a, e);  
  or (y4, y1, y2);  
  or (y_out1, y3, y4);  
  and (y5, b, c);  
  and (y6, b, d);  
  and (y7, b, e);  
  or (y8, y5, y6);  
  or (y_out2, y7, y8);  
endmodule
```



```

module or_nand (y, enable, x1, x2, x3, x4);
  output    y;
  input     enable, x1, x2, x3, x4;

  assign y = ~(enable & (x1 | x2) & (x3 | x4));
endmodule

```

```

module comparator (a_gt_b, a_lt_b, a_eq_b, a, b); // Alternative algorithm
  parameter      size = 2;
  output         a_gt_b, a_lt_b, a_eq_b;
  input          [size: 1] a, b;
  reg            a_gt_b, a_lt_b, a_eq_b;
  integer        k;

  always @ ( a or b ) begin: compare_loop
    for (k = size; k > 0; k = k-1) begin
      if (a[k] != b[k]) begin
        a_gt_b = a[k];
        a_lt_b = ~a[k];
        a_eq_b = 0;
        disable compare_loop;
      end // if
    end // for loop

    a_gt_b = 0;
    a_lt_b = 0;
    a_eq_b = 1;
  end // compare_loop
endmodule

```

```
module comparator (a_gt_b, a_lt_b, a_eq_b, a, b); // Alternative algorithm
```

```
parameter size = 2;
```

```
output a_gt_b, a_lt_b, a_eq_b;
```

```
input [size: 1] a, b;
```

```
reg a_gt_b, a_lt_b, a_eq_b;
```

```
integer k;
```

```
always @ ( a or b ) begin: compare_loop
```

```
for (k = size; k > 0; k = k-1) begin
```

```
if (a[k] != b[k]) begin
```

```
a_gt_b = a[k];
```

```
a_lt_b = ~a[k];
```

```
a_eq_b = 0;
```

```
disable compare_loop;
```

```
end // if
```

```
end // for loop
```


```
a_gt_b = 0;
```

```
a_lt_b = 0;
```

```
a_eq_b = 1;
```

```
end // compare_loop
```

```
endmodule
```

 

# Final issues

---

- Please fill out the student info sheet before leaving
- Come by my office hours (right after class)
- Any questions or concerns?