

EEL 3123C TEST 1 - DURATION: 60 minutes

- 1) Under a unit step input, the output of a circuit is given by $y(t) = \exp(-t)$ for time $t \geq 0$.
Find the steady-state output under input given by $2 \sin(t)$. (40)

For unit step input, $x(t) \Rightarrow X(s) = 1/s$ (5)

$y(t) = \exp(-t) \Rightarrow Y(s) = \frac{1}{s+1}$ (5) $\Rightarrow H(s) = \frac{Y(s)}{X(s)} = \frac{s}{s+1}$ (5)

$H(j\omega) = \frac{j\omega}{j\omega+1} = \frac{\omega}{\omega-j}$ (5) $\Rightarrow |H(j\omega)| = \frac{\omega}{\sqrt{1+\omega^2}}$ (5)


$\theta(j\omega) = +\tan^{-1}\left(\frac{1}{\omega}\right)$ (5)

$y_{s-s} = 2 |H(j1)| \sin(t + \theta(j1))$ (10)
 $= 2 \cdot \frac{1}{\sqrt{2}} \sin(t + \tan^{-1}(1))$
 $= \sqrt{2} \sin(t + 45^\circ)$

- 2) Given $F(s) = \frac{5s^2 + 29s + 32}{s^2 + s - 1}$. Find $\lim_{t \rightarrow 0^+} f(t)$ and $\lim_{t \rightarrow \infty} f(t)$ by using, respectively, the initial and final value theorem if the respective limits exist. (20)

(10) IVT does not apply because $m=n=2$, initial value DNE.
 (10) FVT _____ because system is unstable, one root is in the RHP.

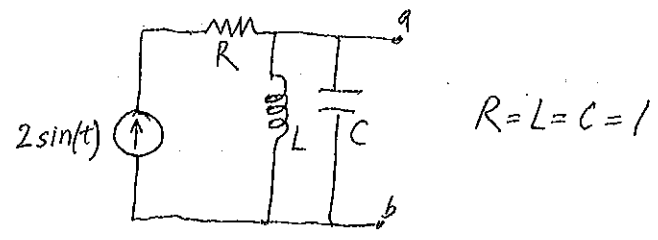3) Looking through terminals a-b, obtain the Thevenin equivalent for the circuit. (30)




$$V_{ab} = I(s) Z(s)$$

$$I(s) = \frac{2}{s^2+1} \quad (5), \quad Z(s) = \frac{1}{sC} \parallel sL = \frac{1}{\frac{1}{s} + s} = \frac{s}{s^2+1}$$

$$V_{ab}(s) = \frac{2s}{(s^2+1)^2} \quad (10)$$

$$Z_{ab} = \frac{s}{s^2+1} \quad (10)$$

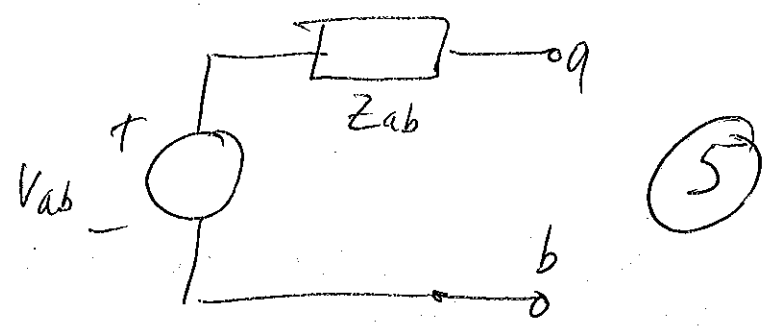

4) Explain the concept of a virtual short for an ideal op-amp. Under what conditions does virtual-short hold? (10)

$V^+ = V^-$ → virtual short (5)
 Holds under negative feedback (5)