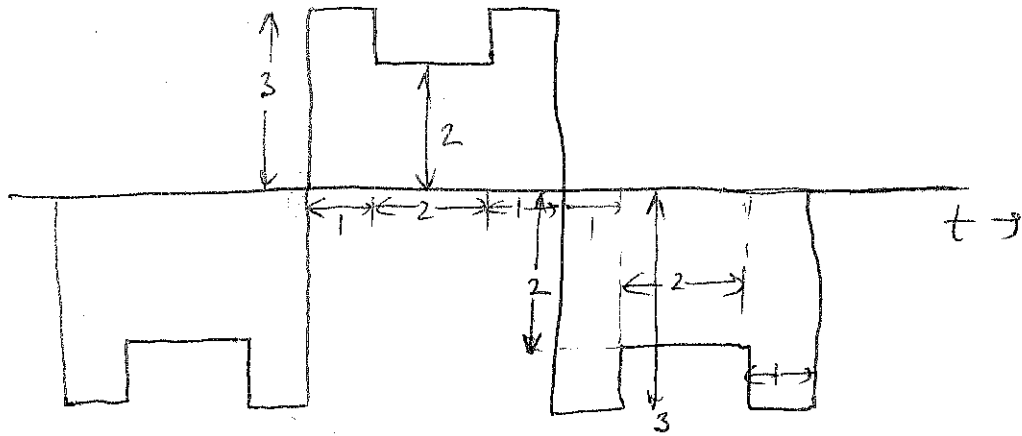


1.





10) What kind of symmetries does the function above show? (Fix $t=0$ to make the function (a) odd, and (b) even) For both cases, use symmetries to calculate a_n , a_k , and b_k with the least amount of computation.

$(12) + (4) + (4) \times \frac{2}{c}$

(60)


2.

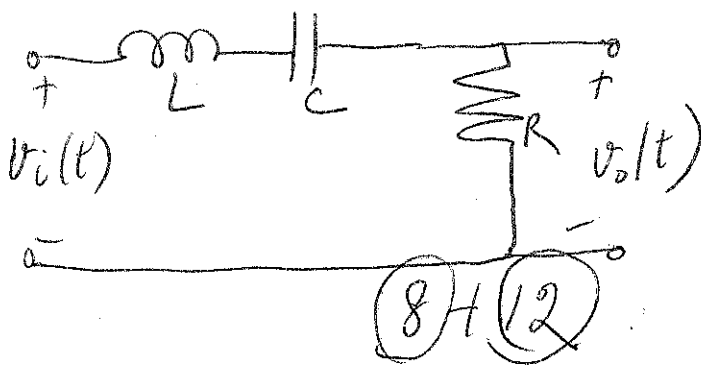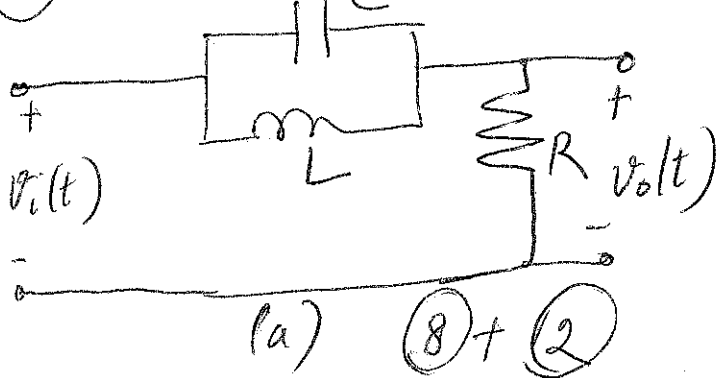

Classify the filters in (a) and (b) as low-pass, high-pass, band-pass, band-stop or none of the above. Give justification based on mathematics and/or circuit element characteristics based reasoning. (40)

Solutions, test 2

11

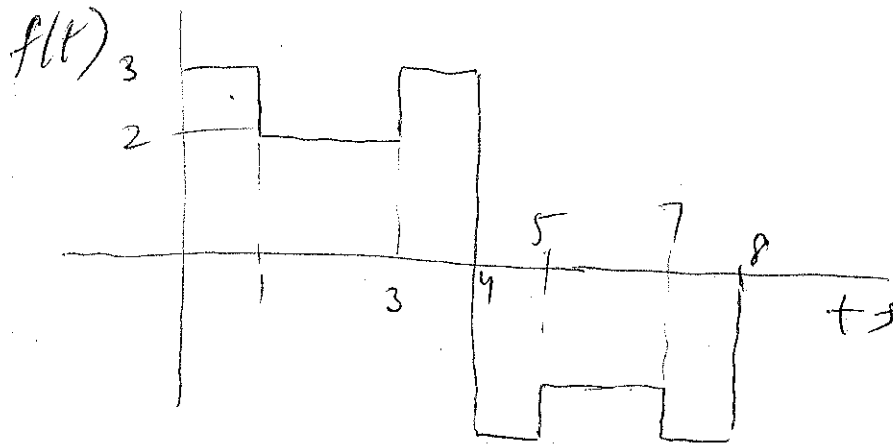Odd Function:

$$a_0 = 0 \quad (\text{odd function})$$

$$a_k = 0 \quad (\text{all } k, \because \text{odd function})$$

$$b_k = 0 \quad (k \text{ even, HW symmetry})$$

$$b_k = \frac{8}{T} \int_0^{T/4} f(t) \sin k \cdot \frac{2\pi}{T} \cdot t \, dt, \quad (k \text{ odd})$$

ω_0 $T = 8$

$$= 1 \int_0^2 f(t) \sin\left(\frac{k \cdot \pi}{4} \cdot t\right) dt$$


$$= \frac{4}{k\pi} \left[3 \cdot \left[\cos\left(\frac{k\pi}{4} \cdot 0\right) - \cos\left(\frac{k\pi}{4} \cdot 1\right) \right] + 2 \left[\cos\left(\frac{k\pi}{4} \cdot 1\right) - \cos\left(\frac{k\pi}{4} \cdot 2\right) \right] \right]$$

$$= \frac{4}{k\pi} \left(3 - \cos\left(\frac{k\pi}{4}\right) - 2 \cos\left(\frac{k\pi}{2}\right) \right)$$

$$= \frac{4}{k\pi} \left(3 - \cos(k\pi/4) \right), \quad k \text{ odd}$$

Even functions:

Soluhms (9.2)

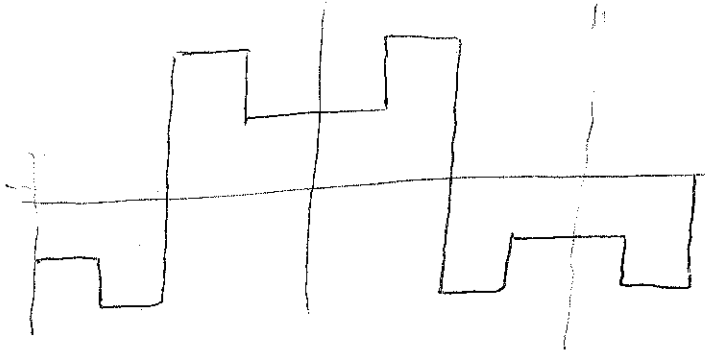

$$a_0 = 0, \quad (HW)$$

$$a_k = 0, \quad (k \text{ even}) \quad (HW)$$

$$a_k = \frac{8}{T} \int_0^{T/4} f(t) \cos k\omega_0 t dt \quad (k \text{ odd})$$

$$= \frac{4}{k\pi} \left[2 \left[\sin\left(\frac{k\pi}{4}\right) - \sin\left(\frac{k\pi}{4}\right) \right] + 3 \left[\sin\left(\frac{k\pi}{2}\right) - \sin\left(\frac{k\pi}{4}\right) \right] \right]$$

$$= \frac{4}{k\pi} \left(2 \sin\left(\frac{k\pi}{4}\right) + 3 \sin\left(\frac{k\pi}{2}\right) \right)$$

$$b_k = 0 \quad \text{for all } k \text{ (even function)}$$

2. (a) is bandstop filter. Equivalent impedance for LC combination is $Z_{eq} = \frac{j\omega L \cdot 1/j\omega C}{j(\omega L - 1/\omega C)}$

$$Z_{eq} = \frac{L/R \times \omega L}{j(\omega^2 LC - 1)} = \frac{-j\omega L}{(\omega^2 LC - 1)}$$

At low and high ω , Z_{eq} is small and input voltage drops across resistor. At $\omega = 1/\sqrt{LC}$, all voltage drops across LC combo and none across resistor.

Solutions (Pg. 3)

~~Thus~~ Thus, there is output voltage at low and high frequencies and small output around the center frequency. Thus, this is a bandpass.

(5) is a bandpass. $Z_{eq} = j(\omega L - \frac{1}{\omega C})$

At low frequencies, input voltage drop across ~~inductor~~ capacitor, at high frequencies, input drops across inductor. Around the center frequency, the inductive and capacitive impedances cancel each other out and most input voltage drops across the resistor.